

Generalisation of Helmholtz-Thèvenin theorem to three-phase electrical circuits

Gheorghe MIHAI

University of Craiova, Faculty of Electrotechnics, Ddul Decebal 5, Romania
E-mail: gmihai@elth.ucv.ro

Abstract. The scope of this paper is to determine the generalized form for equivalent tension generator theorem (Helmholtz-Thèvenin theorem) for three-phase electrical circuit. Any complicated electrical power systems we can reduce depending on any three-phase electrical consumer to a three-phase electrical generator that has certain internal impedance. Starting with this assumption, we have demonstrated the way to obtain the electromotive voltages for an equivalent generator and its internal impedances.

KEYWORDS: Helmholtz-Thèvenin theorem, three-phase electrical circuit.

1. Introduction

From specialized literature is show that a linear and active electrical system, so active linear dipole, can reduce to an electrical generator. Its electromotive voltage is equal with idle running system voltage reporting to **a-b** terminals and its internal impedance equal with measured impedance starting at **a-b** terminals, when the network is passive.

We are starting with following notations, from figure 1.

\underline{U}_{ab0} > The idle running voltage for the linear active dipole reporting to **a-b** terminals.

\underline{Z}_{abp} > The linear impedance of active dipole, looking to **a-b** terminals, then its passive.

\underline{Z} > The charge impedance.

We propose to generalize the Helmholtz-Thèvenin's theorem for a linear active electrical three-phase system, without magnetic couplings, as we see in figure 2.

So, we will demonstrate that we can substitute all three-phase electrical system, looking to terminals consumer, at $\underline{Z}_1, \underline{Z}_2, \underline{Z}_3$ impedance, with three-phase electrical generator, its electromotive voltages are $\underline{U}_{e1}, \underline{U}_{e2}, \underline{U}_{e3}$ and its internal phase -impedance are $\underline{Z}_{i1}, \underline{Z}_{i2}, \underline{Z}_{i3}$, as we see in figure 2.

In these assumptions, we will determinate the parameters of electrical generator in terms of the system' parameters and consumer position.

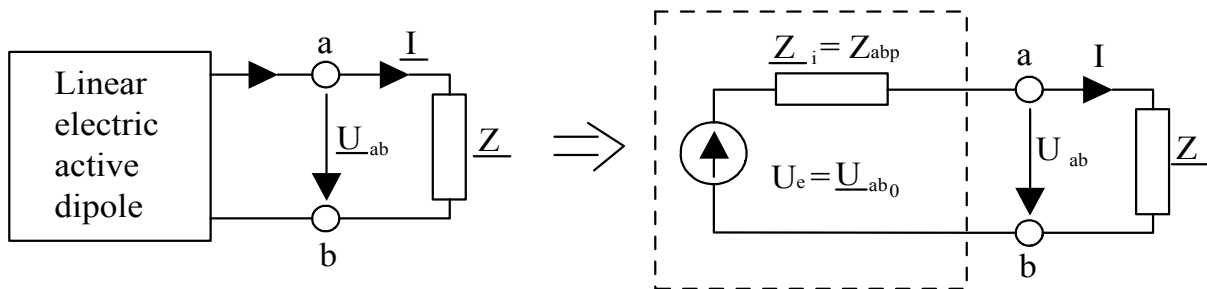


Figure 1. The Helmholtz-Thèvenin's theorem for linear active electrical dipole

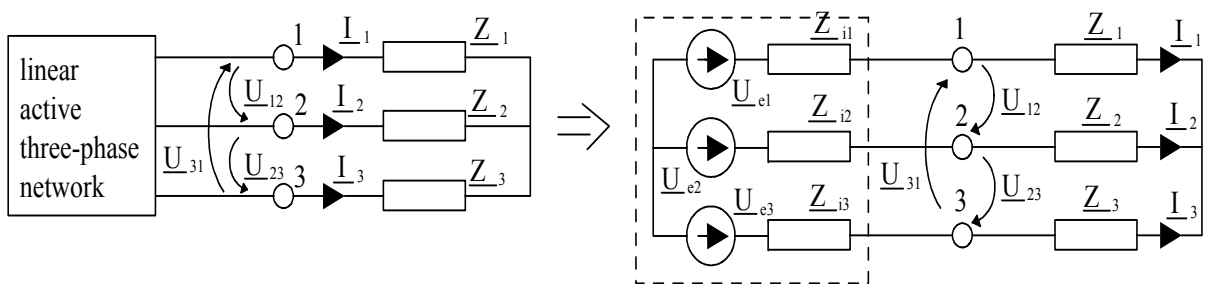


Figure 2. The generalized Helmholtz-Thevenin's theorem for three-phase electrical circuit.

a) an linear three-phase electrical system connected to three-phase consumer

b) an equivalent three-phase electrical generator with the system connected to the same three-phase consumer.

2. The parameters determination for equivalent electrical three-phase generator without null wire

By hypothesis, the electrical three-phase system is linear so, between the terminal voltages and the electrical current of consumer is the relation:

$$\underline{\hat{U}} = \underline{\hat{C}}_1 \underline{\hat{I}} + \underline{\hat{C}}_2 \quad (1)$$

Where:

$$\underline{\hat{U}} = \begin{pmatrix} \underline{U}_{12} \\ \underline{U}_{23} \\ \underline{U}_{31} \end{pmatrix} \quad \underline{\hat{I}} = \begin{pmatrix} \underline{I}_1 \\ \underline{I}_2 \\ \underline{I}_3 \end{pmatrix} \quad \underline{\hat{C}}_1 = \begin{pmatrix} C'_{11} & C'_{12} & C'_{13} \\ C'_{21} & C'_{22} & C'_{23} \\ C'_{31} & C'_{32} & C'_{33} \end{pmatrix} \quad \underline{\hat{C}}_2 = \begin{pmatrix} C_1^2 \\ C_2^2 \\ C_3^2 \end{pmatrix}$$

In order to determine the constant $\underline{\hat{C}}_2$, we will consider the consumer power off, so that the system idles functioning in relation to the consumer:

From relation (1) we obtain:

$$\underline{\hat{C}}_2 = \begin{pmatrix} \underline{U}_{120} \\ \underline{U}_{230} \\ \underline{U}_{310} \end{pmatrix} \quad (2)$$

We can also obtain the current values at consumer equal to zero by electrical way, if the consumer is connected to a linear three-phase auxiliary generator, as we see in figure 3.

The phase currents to consumer are the expressions:

$$\begin{cases} \underline{I}_{1r} = \underline{I}_1 + \underline{I}'_1 = 0 \\ \underline{I}_{2r} = \underline{I}_2 + \underline{I}'_2 = 0 \\ \underline{I}_{3r} = \underline{I}_3 + \underline{I}'_3 = 0 \end{cases} \quad (3)$$

Conforming the superposition principle \underline{I}_{ir} currents from system (3) are obtain from $\underline{I}_1, \underline{I}_2$ and \underline{I}_3 currents do to the system if the auxiliary electrical generator is passive and from $\underline{I}'_1, \underline{I}'_2, \underline{I}'_3$ electrical currents if the system is passive and working only the auxiliary electrical generator, figure 4.

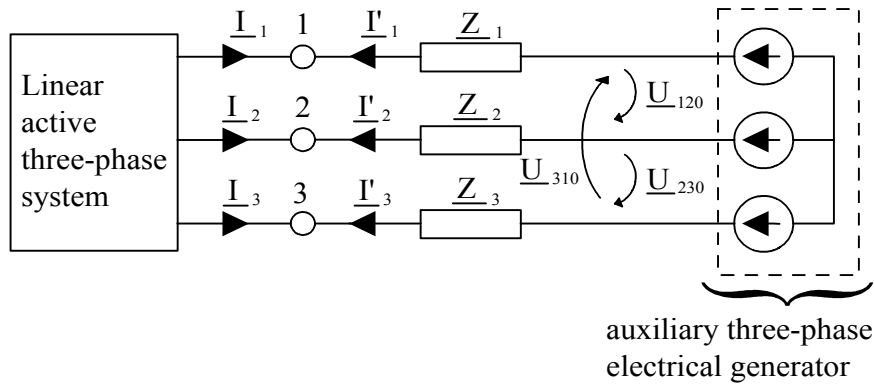


Figure 3. The electrical connection between the consumer and electrical generator

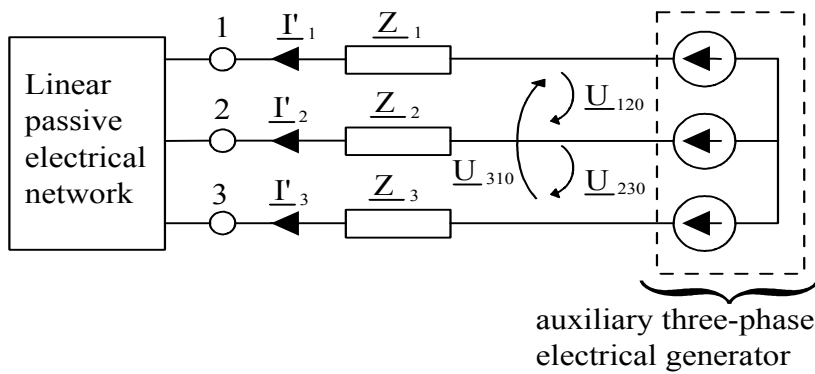


Figure 4. The electrical schema of a passive system and an auxiliary generator that working

We are considered the passive electrical system can be reduce to three impedance in Y connected, figure 5.

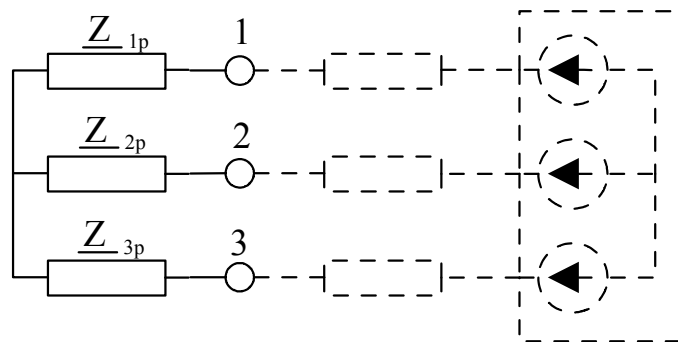


Figure5. The electrical schema of a passive system reduces to three impedance's Y connected.

As we show in figure 6, where are three schema of measuring for the impedance's, in relation with 1, 2 and 3 terminals:

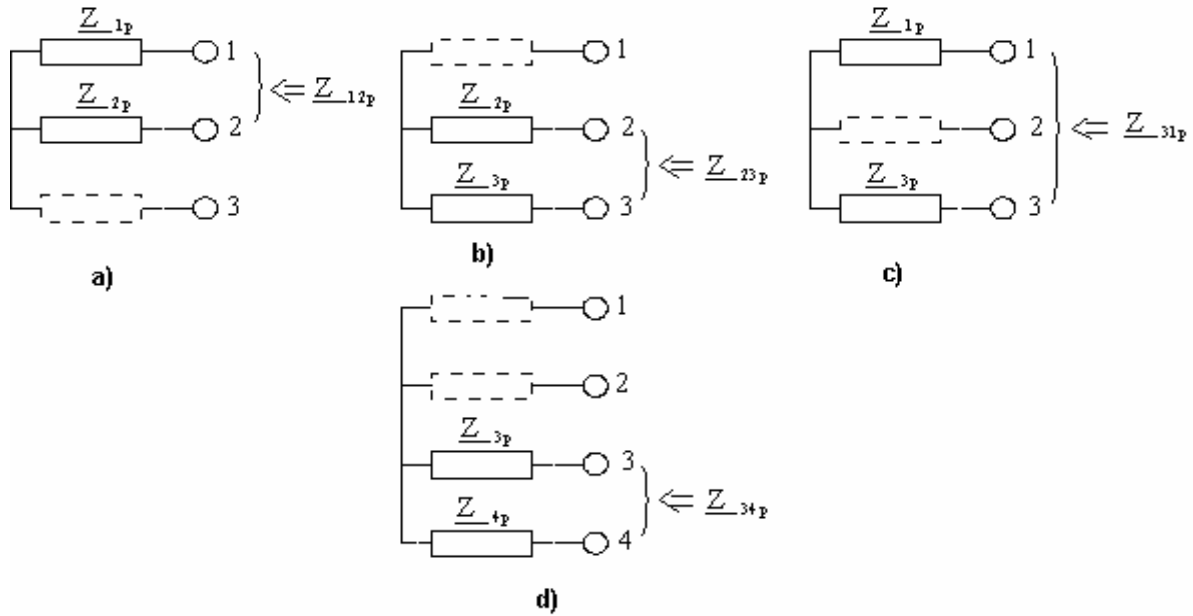


Figure 6. The schema of measuring impedance in relation with 12, 23, 31 and 34 terminals for Y connection.

- in relation with 12 terminals, fig. 6a: $\underline{Z}_{12p} = \underline{Z}_{1p} + \underline{Z}_{2p}$
- in relation with 23 terminals, fig.6b: $\underline{Z}_{23p} = \underline{Z}_{2p} + \underline{Z}_{3p}$
- in relation with 31 terminals, fig.6c: $\underline{Z}_{31p} = \underline{Z}_{3p} + \underline{Z}_{1p}$
- in relation with 34 terminals, fig.6d: $\underline{Z}_{34p} = \underline{Z}_{3p} + \underline{Z}_{4p}$

From the last relations we obtain:

$$\begin{cases} \underline{Z}_{1p} = \frac{\underline{Z}_{12p} - \underline{Z}_{23p} + \underline{Z}_{31p}}{2} \\ \underline{Z}_{2p} = \frac{\underline{Z}_{23p} - \underline{Z}_{31p} + \underline{Z}_{12p}}{2} \\ \underline{Z}_{3p} = \frac{\underline{Z}_{31p} - \underline{Z}_{12p} + \underline{Z}_{23p}}{2} \\ \underline{Z}_{4p} = \underline{Z}_{34p} - \underline{Z}_{3p} \end{cases} \quad (4)$$

From fig.5, we can observe that \underline{Z}_{1p} , \underline{Z}_{2p} and \underline{Z}_{3p} can be consider internal impedance's for auxiliary electrical generator, so:

$$\underline{Z}_{i1} = \underline{Z}_{1p}, \underline{Z}_{i2} = \underline{Z}_{2p}, \underline{Z}_{i3} = \underline{Z}_{3p} \text{ and } \underline{Z}_{i4} = \underline{Z}_{4p} \quad (5)$$

The equivalent electrical generator has:

- the linear electromotive voltage equal to the linear voltage of the idle running system in the considered point:

$$\begin{cases} \underline{U}_{e12} = \underline{U}_{120} \\ \underline{U}_{e23} = \underline{U}_{230} \\ \underline{U}_{e31} = \underline{U}_{310} \end{cases} \quad (6)$$

- the internal phase impedance equal to the passive phase electrical system, see in the considered point, relation(5).

Returning in relation (1), we can observe that $\hat{\underline{C}}_1$ can be obtained from mathematical condition $\hat{\underline{U}} = \mathbf{0}$. This is similar one short-circuit at terminals consumer:

$$\hat{\underline{0}} = \hat{\underline{C}}_1 \hat{\underline{I}}_1 + \hat{\underline{C}}_2 \quad (7)$$

For the schema presented in fig.2b and fig.3 and based on the superposition principle, the network has an equivalent electrical scheme:

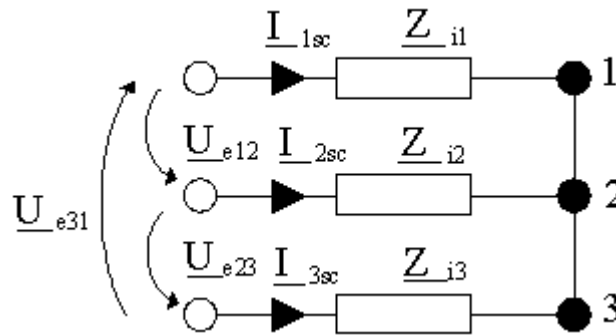


Figure 7. One short-circuits three-phase to the terminals electrical system

From the Kirchoff' second theorem we are obtained:

$$\begin{pmatrix} \underline{U}_{e12} \\ \underline{U}_{e23} \\ \underline{U}_{e31} \end{pmatrix} = \begin{pmatrix} \underline{Z}_{i1} & -\underline{Z}_{i2} & \mathbf{0} \\ \mathbf{0} & \underline{Z}_{i2} & -\underline{Z}_{i3} \\ -\underline{Z}_{i1} & \mathbf{0} & \underline{Z}_{i3} \end{pmatrix} \cdot \begin{pmatrix} \underline{I}_{1sc} \\ \underline{I}_{2sc} \\ \underline{I}_{3sc} \end{pmatrix} \quad (8)$$

From (7) and (8) relations we are obtained:

$$\hat{\underline{C}}_1 = - \begin{pmatrix} \underline{Z}_{i1} & -\underline{Z}_{i2} & \mathbf{0} \\ \mathbf{0} & \underline{Z}_{i2} & -\underline{Z}_{i3} \\ -\underline{Z}_{i1} & \mathbf{0} & \underline{Z}_{i3} \end{pmatrix} = \hat{\underline{Z}}_i \quad (9)$$

That is the internal impedance matrix.

3. The generalization of Helmholtz-Thèvenin formulae for three-phase electrical systems without null wire

From literature we are the linear active dipole formulae:

$$\underline{U}_{ab0} = (\underline{Z} + \underline{Z}_{abp}) \underline{I} \quad (10)$$

Starting with (1), (2), (4), (5) and (9) formula, we are obtained the consumer electrical current relation to an electrical three-phase network:

$$\begin{pmatrix} \underline{U}_{12} \\ \underline{U}_{23} \\ \underline{U}_{31} \end{pmatrix} = \begin{pmatrix} \underline{Z}_1 & -\underline{Z}_2 & \mathbf{0} \\ \mathbf{0} & \underline{Z}_2 & -\underline{Z}_3 \\ -\underline{Z}_1 & \mathbf{0} & \underline{Z}_3 \end{pmatrix} \begin{pmatrix} \underline{I}_1 \\ \underline{I}_2 \\ \underline{I}_3 \end{pmatrix} \quad (11)$$

In matrices form:

$$\underline{\hat{U}} = \underline{\hat{Z}} \underline{\hat{I}} \quad (12)$$

So, to three-phase electrical circuit, (10) formulae become:

$$\underline{\hat{U}}_0 = (\underline{\hat{Z}} + \underline{\hat{Z}}_p) \underline{\hat{I}} \quad (13)$$

Where:

$$\underline{\hat{Z}} = \begin{pmatrix} \underline{Z}_1 & -\underline{Z}_2 & \mathbf{0} \\ \mathbf{0} & \underline{Z}_2 & -\underline{Z}_3 \\ -\underline{Z}_1 & \mathbf{0} & \underline{Z}_3 \end{pmatrix}$$

$$\underline{\hat{Z}}_p = \begin{pmatrix} \underline{Z}_{1p} & -\underline{Z}_{2p} & \mathbf{0} \\ \mathbf{0} & \underline{Z}_{2p} & -\underline{Z}_{3p} \\ -\underline{Z}_{1p} & \mathbf{0} & \underline{Z}_{3p} \end{pmatrix}$$

$$\underline{\hat{U}}_0 = \begin{pmatrix} \underline{U}_{120} \\ \underline{U}_{230} \\ \underline{U}_{310} \end{pmatrix}, \quad \underline{\hat{I}} = \begin{pmatrix} \underline{I}_1 \\ \underline{I}_2 \\ \underline{I}_3 \end{pmatrix}$$

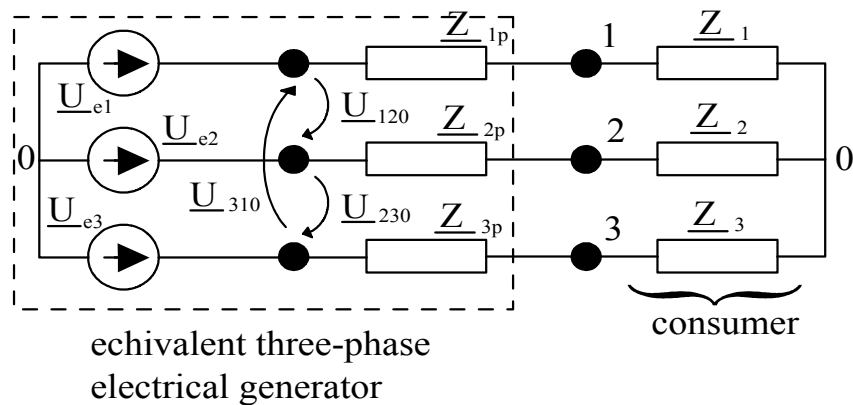


Figure 8. The electrical equivalent schema

The matrix $\underline{\hat{Z}}$ and $\underline{\hat{Z}}_p$ are non-invertible. This property leads to the impossibility to determine the currents to the consumer.

In order to determine the phase, fictitious voltages $\underline{U}_{e1}^*, \underline{U}_{e2}^*, \underline{U}_{e3}^*$ we calculate the center of gravity of the triangle formed by the potentials $\underline{V}_{10}, \underline{V}_{20}, \underline{V}_{30}$ of the phases 1, 2, 3, when let open, fig.9.a.

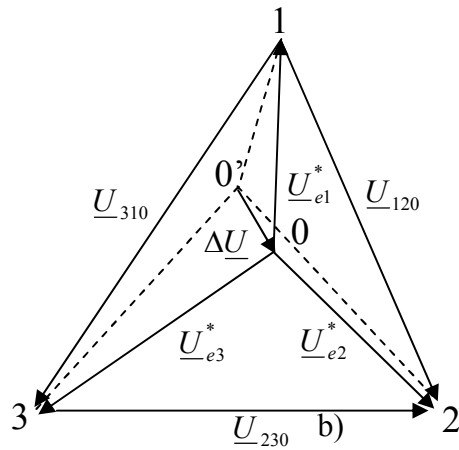
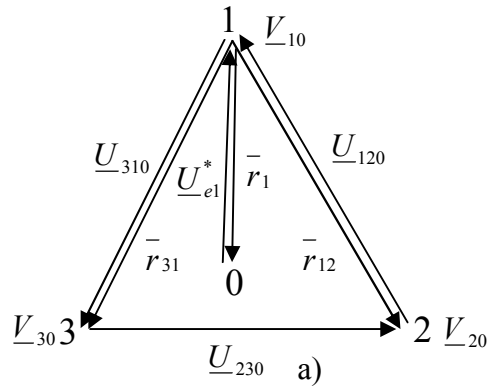


Fig.9. Centre of gravity determinations for the line tensions triangle

The position vector \bar{r}_1 of the centre of gravity O reported to the vertex 1 has the expression:

$$\bar{r}_1 = \frac{1}{3}(\bar{r}_{12} + \bar{r}_{31}) \quad (14)$$

where:

$$\begin{aligned} \bar{r}_1 &= -\underline{U}_{e1}^* \\ \bar{r}_{12} &= -\underline{U}_{120} \\ \bar{r}_{31} &= \underline{U}_{310} \end{aligned} \quad (15)$$

From (14) and (15) relations, we will obtain:

$$\underline{U}_{e1}^* = \frac{1}{3}(\underline{U}_{120} - \underline{U}_{310}) \quad (16)$$

By circular permutations, we can obtain the other phase, fiction phase's voltages:

$$\underline{U}_{e2}^* = \frac{1}{3}(\underline{U}_{230} - \underline{U}_{120}) \quad (17)$$

$$\underline{U}_{e3}^* = \frac{1}{3}(\underline{U}_{310} - \underline{U}_{230}) \quad (18)$$

Neutral displacement of the consumer O' reported to the centre of gravity O, figure 9.b, is given by the relation:

$$\Delta \underline{U} = -\frac{\underline{U}_{e1}^* \underline{Y}_{1t} + \underline{U}_{e2}^* \underline{Y}_{2t} + \underline{U}_{e3}^* \underline{Y}_{3t}}{\underline{Y}_{1t} + \underline{Y}_{2t} + \underline{Y}_{3t}} \quad (19)$$

where:

$$\left\{ \begin{array}{l} \underline{Y}_{1t} = \frac{1}{\underline{Z}_{1p} + \underline{Z}_1} \\ \underline{Y}_{2t} = \frac{1}{\underline{Z}_{2p} + \underline{Z}_2} \\ \underline{Y}_{3t} = \frac{1}{\underline{Z}_{3p} + \underline{Z}_3} \\ \underline{Y}_{4t} = \frac{1}{\underline{Z}_{4p} + \underline{Z}_4} \end{array} \right. \quad (20)$$

The matrix of the phase voltages at the consumer is:

$$\hat{\underline{U}}_{1230} = \begin{pmatrix} \underline{U}_{e1}^* + \Delta \underline{U} & 0 & 0 \\ 0 & \underline{U}_{e2}^* + \Delta \underline{U} & 0 \\ 0 & 0 & \underline{U}_{e3}^* + \Delta \underline{U} \end{pmatrix} \quad (21)$$

The matrix of the internal impedance three-phased electrical generator has the form:

$$\hat{\underline{Z}}_{123p} = \begin{pmatrix} \underline{Z}_{1p} & 0 & 0 \\ 0 & \underline{Z}_{2p} & 0 \\ 0 & 0 & \underline{Z}_{3p} \end{pmatrix} \quad (22)$$

And the one for the three-phased consumer:

$$\hat{\underline{Z}}_{123} = \begin{pmatrix} \underline{Z}_1 & 0 & 0 \\ 0 & \underline{Z}_2 & 0 \\ 0 & 0 & \underline{Z}_3 \end{pmatrix} \quad (23)$$

The electrical three-phase currents we can write them as a diagonal matrix:

$$\hat{\underline{I}}_{123} = \begin{pmatrix} \underline{I}_1 & 0 & 0 \\ 0 & \underline{I}_2 & 0 \\ 0 & 0 & \underline{I}_3 \end{pmatrix} \quad (24)$$

There is dependence between the electrical quantities that can be found in the Thèvenin theorem of the mono-phased, electrical circuits and the ones that can be found in the three-phased, electrical circuits without neutral, given by:

$$\underline{U}_{ab0} \Rightarrow \hat{\underline{U}}_{1230} \quad (25)$$

$$\underline{Z}_{abp} \Rightarrow \hat{\underline{Z}}_{123p}$$

$$\underline{Z} \Rightarrow \hat{\underline{Z}}_{123} \quad (26)$$

$$\underline{I}_{abp} \Rightarrow \hat{\underline{I}}_{123}$$

The Thèvenin theorem for the three-phased, electrical circuits without neutral has the expression:

$$\hat{\underline{U}} = \left(\hat{\underline{Z}}_{123p} + \hat{\underline{Z}}_{123} \right) \hat{\underline{I}}_{123} \quad (27)$$

The above relation generalize Thèvenin theorem of the mono-phased, electrical circuits:

$$\underline{U}_{ab0} = (\underline{Z}_p + \underline{Z})\underline{I}$$

4. Three-phase system with neutral wire

A three-phase system with neutral wire can present in relation with a consumer from four terminal accesses:

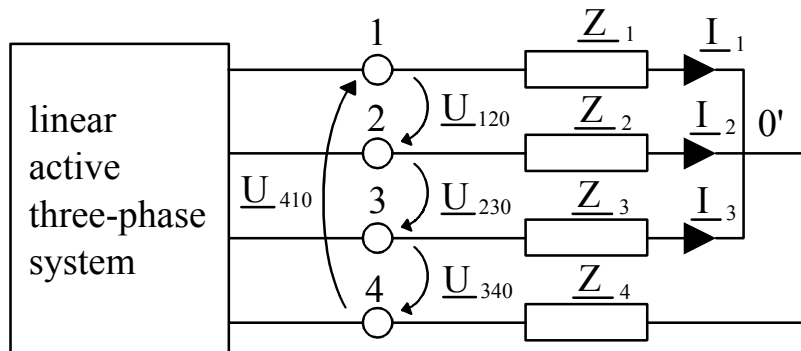


Figure 10. Schema of the linear active three-phase system that is connect to a consumer

These four access terminals 1, 2, 3 and 4' permit to assimilate the system with a multiphase system. The off tensions of the system in relation with the access terminals are \underline{U}_{120} , \underline{U}_{230} , \underline{U}_{340} and \underline{U}_{410} .

In figure 11 is represented the equivalent electrical generator schema that corresponding to the four-access terminals system.

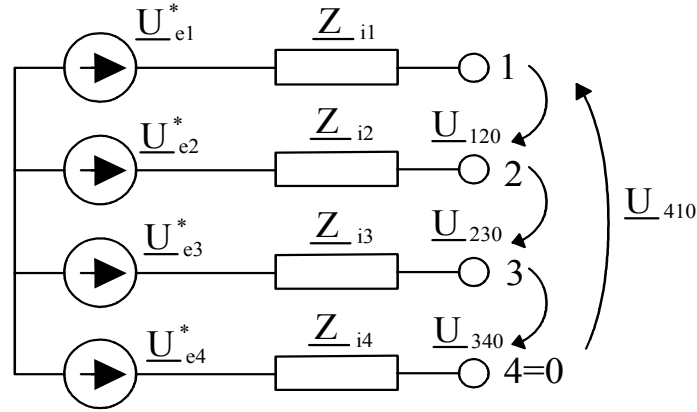


Figure 11. The four-phase equivalent electrical generator schema

In order to determine the phase fiction voltages $\underline{U}_{e1}^*, \underline{U}_{e2}^*, \underline{U}_{e3}^*, \underline{U}_{e4}^*$ we calculate the centre of gravity of the quadrilateral formed by the potentials $\underline{V}_{10}, \underline{V}_{20}, \underline{V}_{30}, \underline{V}_{40}$ of the phases 1, 2, 3, 4 when let open, figure 12, a, b.

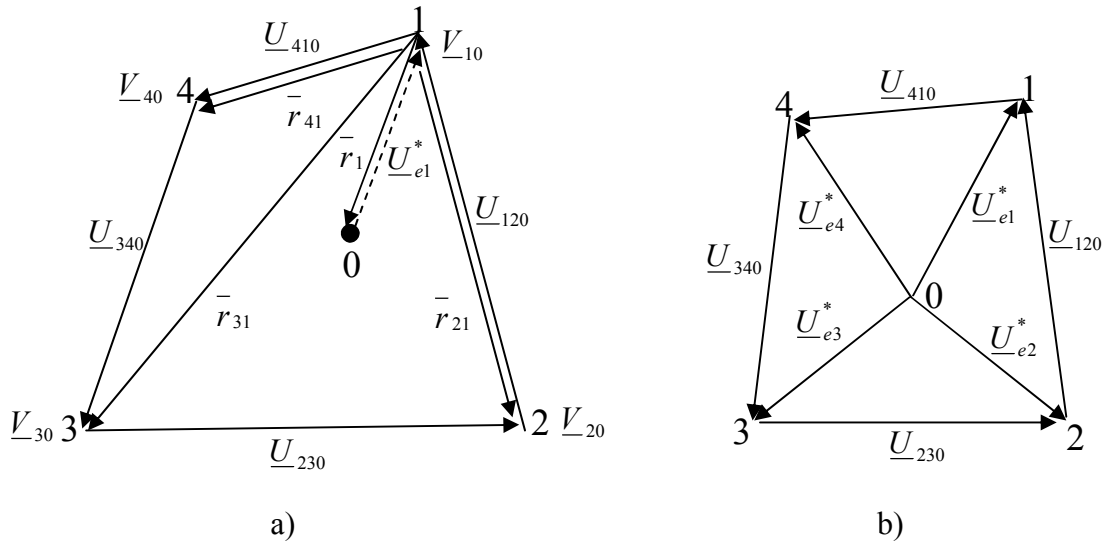


Figure 12. Centre of gravity determination of the quadrilateral

The position vector \bar{r}_1 of the centre of gravity O, reported to the vertex 1 of the quadrilateral has the expression:

$$\bar{r}_1 = \frac{1}{4}(\bar{r}_{21} + \bar{r}_{31} + \bar{r}_{41}) \quad (28)$$

Where:

$$\begin{cases} \bar{r}_1 = -\underline{U}_{e1}^* \\ \bar{r}_{21} = -\underline{U}_{120} \\ \bar{r}_{31} = \underline{U}_{410} + \underline{U}_{340} = -\underline{U}_{230} - \underline{U}_{120} \\ \bar{r}_{41} = \underline{U}_{410} \end{cases} \quad (29)$$

From relations (28) and (29) we obtain (figure 12.a):

$$\underline{U}_{e1}^* = \frac{1}{8}(3\underline{U}_{120} + \underline{U}_{230} - \underline{U}_{340} - 3\underline{U}_{410}) \quad (30)$$

By circular permutations, we can obtain the other fiction phases-voltages:

$$\begin{aligned} \underline{U}_{e2}^* &= \frac{1}{8}(3\underline{U}_{230} + \underline{U}_{340} - \underline{U}_{410} - 3\underline{U}_{120}) \\ \underline{U}_{e3}^* &= \frac{1}{8}(3\underline{U}_{340} + \underline{U}_{410} - \underline{U}_{120} - 3\underline{U}_{230}) \\ \underline{U}_{e4}^* &= \frac{1}{8}(3\underline{U}_{410} + \underline{U}_{120} - \underline{U}_{230} - 3\underline{U}_{340}) \end{aligned} \quad (31)$$

The non-equilibrate consumer, with impedances $\underline{Z}_1, \underline{Z}_2, \underline{Z}_3, \underline{Z}_4$ connected in a star pattern generates the displacement of the neutral electrical potential of the consumer reported to the neutral electrical potential of the generator:

$$\Delta \underline{U} = -\frac{\underline{U}_{e1}^* \underline{Y}_{1t} + \underline{U}_{e2}^* \underline{Y}_{2t} + \underline{U}_{e3}^* \underline{Y}_{3t} + \underline{U}_{e4}^* \underline{Y}_{4t}}{\underline{Y}_{1t} + \underline{Y}_{2t} + \underline{Y}_{3t} + \underline{Y}_{4t}} \quad (32)$$

Analogously to the way we have proceeded in the paragraph 3 we obtain:

$$\hat{\underline{U}}_{12340} = \begin{pmatrix} \underline{U}_{e1}^* + \Delta \underline{U} & 0 & 0 & 0 \\ 0 & \underline{U}_{e2}^* + \Delta \underline{U} & 0 & 0 \\ 0 & 0 & \underline{U}_{e3}^* + \Delta \underline{U} & 0 \\ 0 & 0 & 0 & \underline{U}_{e4}^* + \Delta \underline{U} \end{pmatrix} \quad (33)$$

$$\hat{\underline{Z}}_{1234p} = \begin{pmatrix} \underline{Z}_{1p} & 0 & 0 & 0 \\ 0 & \underline{Z}_{2p} & 0 & 0 \\ 0 & 0 & \underline{Z}_{3p} & 0 \\ 0 & 0 & 0 & \underline{Z}_{4p} \end{pmatrix} \quad (34)$$

$$\hat{\underline{Z}}_{1234} = \begin{pmatrix} \underline{Z}_1 & 0 & 0 & 0 \\ 0 & \underline{Z}_2 & 0 & 0 \\ 0 & 0 & \underline{Z}_3 & 0 \\ 0 & 0 & 0 & \underline{Z}_4 \end{pmatrix} \quad (35)$$

$$\hat{\underline{I}}_{1234} = \begin{pmatrix} \underline{I}_1 & 0 & 0 & 0 \\ 0 & \underline{I}_2 & 0 & 0 \\ 0 & 0 & \underline{I}_3 & 0 \\ 0 & 0 & 0 & \underline{I}_4 \end{pmatrix} \quad (36)$$

In the above relations, $\underline{U}_{ei}, i=1,2,3,4$, have the forms (30) and (31), $\Delta \underline{U}$ has the form (32), $\underline{Z}_{ip}, i=1,2,3,4$ have the forms (20).

For electrical three-phase circuits with neutral, the Thèvenin theorem has the form:

$$\hat{\underline{U}} = \left(\hat{\underline{Z}}_{1234p} + \hat{\underline{Z}}_{1234} \right) \hat{\underline{I}}_{1234} \quad (37)$$

5. Conclusions

1. The Helmholtz – Thèvenin theorem for a linear active dipole may be generalized to a linear active three-phase system.
2. The obtained formula (27) and (37) generalized the Helmholtz –Thevenin' theorem.
3. The system currents determination its make by transformation Δ - \mathbf{Y} .

REFERENCES

- [1] Pl.Andronescu, *Electrotechnics Bases*, vol.II, Ed. Didactica si Pedagogica, Bucuresti, 1972.
- [2] K.Simonyi, *Theoretical Electrotechnics*, Ed. Tehnica, Bucuresti, 1974.
- [3] I.Antoniou, *Electrotechnics Bases*, vol.II, Ed. Didactica si Pedagogica, Bucuresti, 1974.
- [4] A.Timotin, *Lessons Electrotehnics Bases*, Ed. Didactica si Pedagogica, Bucuresti, 1970.