A Feasible Design of Elementary Quantum Arithmetic Logic Units for Near-Term Quantum Computers

Junxu Li^{1,*}

¹Department of Physics, College of Science, Northeastern University, Shenyang 110819, China (Dated: September 20, 2024)

Quantum arithmetic logic units (QALUs) constitute a fundamental component of quantum computing. However, the implementation of QALUs on near-term quantum computers remains a substantial challenge, largely due to the limited connectivity of qubits. In this paper, we propose feasible QALUs, including quantum binary adders, subtractors, multipliers, and dividers, which are designed for near-term quantum computers with qubits arranged in two-dimensional arrays. Additionally, we introduce a feasible quantum arithmetic operation to compute the two's complement representation of signed integers. The proposed QALUs utilize only Pauli-X gates, CNOT gates, and $C\sqrt{X}$ (CSX) gates, and all two-qubit gates are operated between nearest neighbor qubits. Our work demonstrates a viable implementation of QALUs on near-term quantum computers, advancing towards scalable and resource-efficient quantum arithmetic operations.

I. INTRODUCTION

Quantum computing represents a paradigm shift in computational capabilities. The unitary quantum operations affect simultaneously each element of the superposition, facilitating extensive parallel data processing within a singular quantum hardware[1]. By leveraging superposition and entanglement, quantum computers usher in unprecedented computational capabilities, and can efficiently solve some classically intractable problems [2–18]. The best known example is Shor's algorithm[19], which is designed to find the prime factors of a large composite integer. Besides, quantum states that are easily prepared with a quantum computer exhibit properties beyond classical capabilities [20–23], and no known classical algorithm has been able to simulate a quantum computer to date [10].

At the core of this transformative technology are quantum arithmetic logic units (QALUs), which perform essential arithmetic operations such as addition, subtraction, multiplication, division, and modular exponentiation within a quantum framework[24, 25]. Classical computing relies on arithmetic logic units (ALUs) to execute basic arithmetic operations [26, 27]. Similarly, QALUs serve as the building blocks for more complex computations and algorithms in quantum computing. For example, the quantum modular arithmetic is integral to the Shor's factoring algorithm[19]. In this context, the efficiency of QALUs is directly correlated with the overall performance of the quantum algorithm. The creation of efficient and practical QALUS is essential for unlocking the full potential of quantum computing, paving the way for efficient quantum algorithms and applications [28, 29]. Research on quantum arithmetic circuits is not only

of theoretical significance but also poised to drive technological breakthroughs and innovative applications.

Thus, there is a broad range of studies in the existing literature which tackle the design of QALUs for quantum systems, and it is still of great interest in developing novel designs and refining the existing ones.

A primary design method of QALUs utilizes the Clifford gates and T gates sets[30]. The first QALUs were reversible versions of known classical implementations [24, 25]. In 1996, Vedral and coworkers explicitly constructed several quantum elementary arithmetic operations using Clifford gates and T gates [24], including the first quantum ripplecarry adder and the quantum modular exponentiation, which is a significant landmark in the development of quantum arithmetic. To perform binary addition on quantum computers, researchers have proposed and developed various quantum adders based on ripple-carry[24, 31, 32], carry-lookahead[33, 34], carry-save[35], and hybrid[28, 36] structures. The quantum binary subtractors have structures closely resembling those of quantum adders, and the typical quantum subtractors are implemented based on ripple-borrow subtraction method[37–39]. In the domain of multiplication, various Clifford and T gates based quantum multipliers are proposed, leveraging the typical multiplication methods including long multiplication[40-42], Karatsuba[43, 44], Toom-Cook[45, 46], and Wallace Tree[47, 48] algorithms. Recently, inspired by classical division algorithms, such as long division and Goldschmidt algorithm, several quantum dividers are also presented using Clifford and T gates [47, 49-51]. In these QALUs, Toffoli gates play a vital role. To standardize and compare various quantum designs, the T gate cost is frequently discussed, particularly at the level of the Toffoli gate [52]. While Clifford gates are relatively straightforward to implement

^{*} Emial: lijunxu1996@gmail.com

and exhibit lower error rates, T gates are more complex and costly, making their optimization crucial for the efficient design of quantum circuits. Circuits designed with this method can exploit advanced fault-tolerant architectures based on quantum errorcorrecting codes, such as the surface code[53], to address critical challenges such as the fragility of quantum states and susceptibility to external noise.

Another significant arithmetic framework is based on the quantum Fourier transform (QFT)[54, 55]. QFT-based quantum arithmetic circuits typically commence with a QFT block that converts the input state to the frequency domain, performs arithmetic operations using controlled phase gates, and then reverts the state to the original domain through an inverse Fourier transform. With assistance of the QFT, a variety of fast integer arithmetic operations are developed, including QFT-based quantum adders[37, 56], subtractors[57, 58], multipliers[57, 59] and dividers[60]. This approach leverages efficient operations in the Fourier basis to streamline arithmetic operations, particularly in scenarios requiring multiplication and exponentiation[29].

Despite advancements in quantum computing, the implementation of QALUs on near-term quantum computers remains challenging One inevitable obstacle is the implementation of Toffoli gates, which are crucial in QALUs based on Clifford and T gates. Experimentally, achieving high-fidelity Toffoli gates is exceedingly difficult, even for a linear chain of three qubits[61]. A Toffoli gate can be decomposed into single- and two-qubit gates. The decomposition requires at least five two-qubit gates for fully connected qubits[62, 63], and eight for nearest-neighbor connected qubits[64]. The complexity increases further when Toffoli gates involve qubits that are not physically connected [65, 66]. Another obstacle is the implementation of two- or multi-qubit gates among the remote qubits [67, 68]. In existing QALUs, there are often two-qubit or multi-qubit gates that involve qubits which are not physically connected. In many quantum computing architectures, qubits are arranged in physical layouts where not all qubits are directly connected [22, 69, 70]. Consequently, twoqubit gates are typically executed on qubits that are physically adjacent. The limited connectivity of native qubits poses a significant hindrance to the implementation of quantum algorithms that necessitate long-range interactions.

To address these issues, this paper presents elementary quantum arithmetic logic units (QALUs), including quantum adders, subtractors, multipliers, and dividers, designed for near-term quantum computers. The proposed QALUs can be implemented using only Pauli-X gates, CNOT gates, and $C\sqrt{X}$ gates,with all two-qubit gates operating on neighboring qubits. Thus, the proposed QALUs are feasible for implementation on near-term quantum computers where qubits are organized in two-dimensional arrays, such as Sycamore[22] and Zuchongzhi[70].

The rest of the paper is organized as follows. In Sec.(II), we introduce scalable quantum full adders (denoted as P_I, P_{II}), where input terms are mapped to two qubit columns and the output sum is mapped to another column. Additionally, we present a special quantum adder (denoted as P_{III}) optimized for iterative additions. For subtraction, in Sec.(III), we present the quantum operation that compute the two's complement representation of signed binary integers, and demonstrate how to perform subtraction with quantum adders in the two's complement representation. Inspired by the principles of long multiplication and long division, we then present quantum multipliers and quantum dividers in Sec.(6) and Sec.(V). For simplicity, in Sec.(II, III, 6, V) we assume that the input states are some certain states in the computational basis. In Sec.(VI), we explicitly demonstrate that the proposed QALUs also support superposition states as input. Our conclusions are presented in Sec.(VII).

II. QUANTUM ADDERS

A. Quantum One-bit Full Adder

Addition is a fundamental operation that serves as a cornerstone for the functionality of all algorithms built upon it. In classical electronics, adders, or summers, are digital circuits that perform addition of binary numbers[26, 27]. In 1937, Claude Shannon firstly demonstrated binary addition in his graduate thesis[71]. One-bit full adder adds three inputs and produces two outputs. The first two inputs are single binary digits a and b, and the third input is an input carry, denoted as c_{in} . The carry digit represents an overflow into the next digit of a multi-digit addition. The two outputs are sum s and carry c_{out} , where $a + b + c_{in} = s + 2c_{out}$. A full adder performs binary addition as

$$s = a \oplus b \oplus c_{in} \tag{1}$$

$$c_{out} = (a \cdot b) + (c_{in} \cdot (a \oplus b)) \tag{2}$$

Traditionally, addition algorithms designed for a quantum computer have mirrored their classical counterparts [24, 25]. One possible implementation of quantum one-bit full adder is depicted in Fig.(1), which is implemented with only Toffoli gates and CNOT gates. There are 4 qubits, 2 qubits for the binary digits a and b, and the other 2 qubits for the carry and the sum. The input c_{in} is converts into sas output, whereas c_{out} takes the place of c_{in} in the next digit of a multi-digit addition.



FIG. 1: One typical implementation of a one-bit full adder with Toffoli gates and CNOT gates.

There are 4 qubits, 2 qubits for the binary digits a and b, and the other 2 qubits for the carry and the sum.

The input c_{in} is converts into s as output, whereas c_{out} takes the place of c_{in} in the next digit of a multi-digit addition.

In the quantum adder as shown in Fig.(1), there are two Toffoli gates. However, it is experimentally challenging to implement high-fidelity Toffoli gates, and it is hardly feasible to implement multi-digit addition based on this design on near-term quantum computers.

To address this issue, here we present a feasible and scalable quantum full-adder, which can be decomposed into Pauli-X gates, $C\sqrt{X}$ gates and CNOT gates, and all two-qubit gates are only applied on the nearest-neighbor qubits. Therefore, it is feasible to implement the proposed quantum adder on near-term quantum computers, where the qubits are assigned in two-dimensional arrays.

A quantum one-bit full adder performs the binary addition as shown in Eq.(1) and Eq.(2), which can be rewritten as,

$$|s\rangle = X^{a \oplus b} |c_{in}\rangle \tag{3}$$

$$|c_{out}\rangle = X^{a \oplus b \oplus c_{in} + \frac{1}{2}(a \oplus b + a \oplus c_{in} + b \oplus c_{in})}|0\rangle \qquad (4)$$

where X is the Pauli-X gate, and $X^{1/2}$, often denoted as \sqrt{X} or SX gate, is the square root of X,

$$\sqrt{X} = \frac{1}{2} \begin{bmatrix} 1+i & 1-i \\ 1-i & 1+i \end{bmatrix}$$
(5)

According to Eq.(3,4), there are at least 4 qubits in a quantum one-bit full adder. Two qubits denoted as A, B for the inputs a, b, one qubit denoted as C for the input carry c_{in} and output s, and one qubit denoted as C' for the output carry c_{out} . States of qubits A, B remains unchanged in the addition operation.

Here we present two designs of quantum one-bit one bit full adders, and in Fig.(2a,b) we present the corresponding qubit connectivity, where squares represent physical qubits and edges are the allowed interactions. A cascade of these quantum one-bit full adders forms quantum adders for multiple bits, and the corresponding qubit connectivity is depicted



FIG. 2: Required qubit and their connectivity for the proposed quantum adders. Squares in the graph represent physical qubits and edges are the allowed interactions. (a, b) Qubit connectivity for 2-bit quantum full adder. Inputs a, b are mapped onto qubits A, B, c_{in} is mapped onto qubit C. Qubits C', C'' are initialized at state $|0\rangle$. After the applying the circuits of quantum full adder, the state of qubit Cindicates the sum s, whereas state of C' indicates the output carry c_{out} . C'' is ancilla qubit. (c, d) Quantum adders supporting multiple bits, which are cascades of one-bit full adders as shown in (a) and (b). In (a, c), the outputs are at stored in the middle column, whereas in (b, d) the outputs are stored in the side column.

in Fig.(2c,d). Details about quantum adders for multiple bits are later discussed in Sec.(IIB). In Fig.(2a,c) the two inputs are not physically connected, and the outputs are stored in the center column. In Fig.(2b,d) the two inputs are connected, whereas the outputs are stored in the side column. In Fig.(2a,b), qubit C'' is ancilla qubit, which is initialized at state $|0\rangle$ and is still at state $|0\rangle$ after the full addition operation. For simplicity, we denote the one-bit full adders in Fig.(2a,b) as \hat{P}_I , \hat{P}_{II} , and the corresponding adders for multiple bits as P_I , P_{II} .

Consider the situation where the outputs in the middle columns as depicted in Fig.(2a). There are 5 qubits denoted as A, B, C, C', C'', and the edges are the allowed interactions between the nearest-neighbor qubits. In Fig.(3) we present the corresponding quantum one-bit full adder. There are in total 20 two-qubit gates, including 17 CNOT gates and $3 C\sqrt{X}$ gates. All of these two-qubit gates are

applied between nearest-neighbor qubits as depicted in Fig.(2a). Thus, \hat{P}_I can be implemented on nearterm quantum computers, where the qubits are assigned in two-dimensional arrays.

In Tab.(I) we present the quantum states evolution when applying \hat{P}_I , where ϕ corresponds to the stages marked by the dashed lines in Fig.(3). Initially, inputs a, b are mapped to qubits A, B, and the input carry c_{in} is mapped to qubit C. Qubits C' and C'' are initialized at state $|0\rangle$. For simplicity, the overall quantum states are written as a separable form as shown in Tab.(I), where the inputs $a, b, c_{in} \in \{0, 1\}$. The first step is to implement operation $X^{\frac{1}{2}a\oplus b}$, corresponding to the operations before $|\phi_I\rangle$ in Fig.(3). Recalling the qubit connectivity as shown in Fig. (2a), qubits A and B are not physically connected. Notice that $c_{in} \oplus (a \oplus b \oplus c_{in}) = a \oplus b$, here we alternatively prepare qubit C' at state $|a \oplus b\rangle$ by the first 4 CNOT gates. Next, a $C\sqrt{X}$ gate is applied, where C' is control qubit and C'' is the target. Then the 4 CNOT gates are applied in the inverse order, converting C' and C'' to the initial state. The second step is to swap the state $X^{\frac{1}{2}a\oplus b}|0\rangle$ to qubit C', according to the two CNOT gates between ϕ_I and ϕ_{II} . Generally, a SWAP gate contains three CNOT gates. Here the initial state of C' is $|0\rangle$, thus we only need two CNOT gates to swap the state of qubits C' and C''. Since then we will add no more operations on ancilla qubit C''. Ancilla qubit C'' keeps state $|0\rangle$ till the end. The third step is to implement operation $X^{\frac{1}{2}a \oplus c_{in}}$, corresponding to the operations between ϕ_{II} and ϕ_{III} . Similarly, the forth step is to implement operation $X^{\frac{1}{2}b\oplus c_{in}}$, corresponding to the operations between ϕ_{III} and ϕ_{IV} . The final step is to prepare the $a \oplus b \oplus c_{in}$ terms, corresponding to the three CNOT gates after ϕ_{IV} . The first two CNOT gates converts C from $|c_{in}\rangle$ to $|a \oplus b \oplus c_{in}\rangle$, and the last CNOT gate implements $X^{a \oplus b \oplus c_{in}}$ on qubit C'. As X and \sqrt{X} gates commute, the output state of C and C' are the sum sand output carry $c_o ut$ in two-bit binary addition, as described in Eq.(3, 4).

The quantum one-bit full adder in Fig.(3) is denoted as $\hat{P}_I(A, B, C, C', C'')$, where P indicates that the circuit is designed for addition operation (plus), subscript I indicates that this is the first type quantum adder, the hat notation indicates that this is one-bit quantum adder. For clarity, the involved qubits, A, B, C, C', C'', are also included in the notation. The computational basis can be expressed as a five-digit binary string, which corresponds to these five qubits. We have

$$\hat{P}_{I}(A, B, C, C', C'')|a, b, c_{in}, 0, 0\rangle = |a, b, s, c_{out}, 0\rangle$$
(6)

where the outputs s, c_{out} are given in Eq.(1,2).

. ...

In the quantum one-bit full adder as shown in Fig.(3), qubits A, B that represent the inputs are

not physically connected, and the outputs are stored in the middle column. The qubits might be assigned in other architectures. Consider the situation as depicted in Fig.(2b), where the qubits A, B are neighbors, and only B directly connects to qubit C, which is initialized as the input carry $|c_{in}\rangle$. Similarly, there are 5 qubits denoted as A, B, C, C', C'', and the edges in Fig. (2b) represent the allowed interactions between the neighbors. The quantum states at certain stages are exactly the same as presented in Tab.(I), where ϕ indicate the stages marked by the dashed lines in Fig.(4).

We denote the quantum one-bit full adder as shown in Fig.(4) as $\hat{P}_{II}(A, B, C, C', C'')$, indicating the second type quantum adder. Similarly, we have

$$\hat{P}_{II}(A, B, C, C', C'')|a, b, c_{in}, 0, 0\rangle = |a, b, s, c_{out}, 0\rangle$$
(7)

As qubit A is not directly connected to qubit C, here additional CNOT gates are necessary to implement the operations such as $X^{\frac{1}{2}a \oplus c_{in}}$. Thus, the quantum full-adder in Fig.(4) requires more CNOT gates. In total, the quantum one-bit full-adder in Fig.(4) can be decomposed into 22 CNOT gates and 3 $C\sqrt{X}$ gates, whereas the implementation in Fig.(3) requires 17 CNOT gates and 3 $C\sqrt{X}$ gates. Notice that there are repeating CNOT pairs at the left and right of the dashed line ϕ_{IV} in Fig.(3), and at the left and right of ϕ_{III} in Fig.(4). These CNOT pairs cancel out and can be deleted in the final implementation. Therefore, the proposed quantum one-bit fulladder requires 15 CNOT gates and 3 $C\sqrt{X}$ gates with the implementation in Fig.(3), or 20 CNOT gates and 3 $C\sqrt{X}$ gates with the implementation in Fig.(4).

Standard Quantum Adders Supporting В. **Multiple Bits**

In classical computers or processors, the one-bit full adder is usually a component in a cascade of adders that adds multiple bit numbers. Similarly, it is possible to create a quantum adder that supports multiple bits by cascading multiple one-bit full adders. In this section, we propose the design of quantum adder that adds two given integers. The inputs are two N-bit binary integers, and the output is a (N+1)-bit binary integer. The inputs are mapped to 2N qubits, and the output is stored in N+1 qubits. Additionally, one extra ancilla qubit is involved in the quantum adder. Thus, 3N+2 qubits are required in total.

Consider 3N + 2 qubits as depicted in Fig.(2c,d), where the squares represent physical qubits and edges are the allowed interactions. The Nqubits denoted as A_{N-1}, \dots, A_0 are initialized as $|a_{N-1}\cdots a_0\rangle$, corresponding to the input integer in



FIG. 3: Implementation of quantum one-bit full adder \hat{P}_I , corresponding to the qubit connectivity in Fig.(2)a. There are 5 qubits, 2 qubits denoted as A, B for the binary digits a and b, 2 qubits C and C' for the carry and the sum, and qubit C'' as ancilla qubit. Initially, inputs a, b are mapped to qubits A, B, and the input carry c_{in} is mapped to qubit C. Qubits C' and C'' are initialized at state $|0\rangle$.

TABLE I: Overall quantum states at certain stages in the quantum one-bit full adder, ϕ corresponds to the dashed lines marked in Fig.(3) and Fig.(4).

Overall quantum state					
Stage	Qubit				
	А	В	\mathbf{C}	\mathbf{C}	C"
Initial	$ a\rangle$	$ b\rangle$	$ c_{in} angle$	$ 0\rangle$	$ 0\rangle$
ϕ_I	a angle	b angle	$ c_{in} angle$	0 angle	$X^{\frac{1}{2}a\oplus b} 0\rangle$
ϕ_{II}	a angle	b angle	$ c_{in} angle$	$X^{\frac{1}{2}a\oplus b} 0\rangle$	0 angle
ϕ_{III}	a angle	b angle	$ c_{in} angle$	$X^{\frac{1}{2}(a\oplus b+a\oplus c_{in})} 0\rangle$	0 angle
ϕ_{IV}	a angle	b angle	$ c_{in} angle$	$X^{\frac{1}{2}(a\oplus b+a\oplus c_{in}+b\oplus c_{in})} 0\rangle$	0 angle
Final	a angle	\ket{b}	$\ket{a\oplus b\oplus c_{in}}$	$X^{a \oplus b \oplus c_{in} + \frac{1}{2}(a \oplus b + a \oplus c_{in} + b \oplus c_{in})} 0\rangle$	0 angle

N-digit binary form $(a_{N-1} \cdots a_0)_{bin}$, where a_{N-1} is the highest digit and a_0 is the lowest digit. Similarly, the N qubits denoted as B_{N-1}, \cdots, B_0 are initialized as $|b_{N-1} \cdots b_0\rangle$, corresponding to the input integer in N-digit binary form $(b_{N-1} \cdots b_0)_{bin}$. The N + 2 qubits qubits denoted as C_{N+1}, \cdots, C_0 are all initialized as ground state $|0\rangle$.

The quantum multi-bit adder can be implemented as a chain of cascaded quantum one-bit full adders. The first step is the addition of the lowest digit. 5 qubits are included in the one-bit addition: A_0, B_0, C_0, C_1, C_2 . Qubits A_0 and B_0 corresponds to the inputs a_0 and b_0 , which are the least significant bits (LSB) of the inputs. The input carry c_{in}^0 for the addition of lowest digit is 0, thus qubit C_0 is initialized as $|0\rangle$ at the beginning. Qubits C_1, C_2 are also initialized as $|0\rangle$. The superscripts of the input carry and output carry indicate the corresponding order of digit. For instance, in the addition of the LSB, the input carry is denoted as c_{in}^0 , and the output carry is denoted as c_{out}^0 . To add the LSB, apply the quantum one-bit full adder \hat{P}_I or \hat{P}_{II} as presented in Sec.(IIA). Qubits A_0 , B_0 do not change in the addition. Qubit C_0 is converted to state $|s_0\rangle$, where s_0 is the output sum of a_0 and b_0 . Qubit C_1 is

converted to $|c_{out}^0\rangle$, corresponds to the output carry in addition of a_0 and b_0 . The ancilla qubit C_2 is still at state $|0\rangle$.

Then consider the addition of the next digit, a_1 , b_1 , along with input carry c_{in}^1 . In multi-bit addition, the output carry in the addition of n^{th} digit is the input carry in the addition of $(n+1)^{th}$ digit. Here qubit C_1 is converted to $|c_{out}^0\rangle$ after the addition of a_0, b_0 , where c_{out}^0 is also the input carry c_{in}^1 for the addition of a_1, b_1 . Thus after the addition of a_0, b_0 , we have qubits A_1, B_1, C_1 at the appropriate state corresponding to the inputs for the addition of a_1 , b_1 . Apply the quantum one-bit full adder \hat{P}_I or \hat{P}_{II} on qubits A_1, B_1, C_1, C_2, C_3 . Qubit C_1 is converted to state $|s_1\rangle$, where s_1 is the output sum of a_1 and b_1 . Qubit C_2 is converted to $|c_{out}^1\rangle$, corresponds to the output carry in addition of a_1 and b_1 . The ancilla qubit C_3 is still at state $|0\rangle$.

By iteratively adding each bit, we apply the quantum one-bit full adder N-2 times, from the less significant bit to the more significant ones. By the end, after the addition of the most significant bit (MSB), qubit C_N is converted to state $|c_{out}^{N-1}\rangle$, corresponding to the output carry in addition of a_{N-1} and b_{N-1} . There is already no more higher order



FIG. 4: Implementation of quantum one-bit full adder \hat{P}_{II} , corresponding to the qubit connectivity in Fig.(2b). The quantum states at certain stages are exactly the same as presented in Tab.(I), where ϕ indicate the stages marked by the dashed lines.

digits in the inputs. Thus, the output carry c_{out}^{N-1} is just the MSB in the input sum, and denoted as s_N for simplicity. Therefore, the state of qubits C_N, \dots, C_0 corresponds to the output, a (N + 1)-bit binary integer. As for the ancilla qubit C_{N+1} , it keeps state $|0\rangle$ after the addition of two input N-bit binary integers.

We present in Alg.(1) the algorithm to implement quantum adders supporting multiple bits, where the notation \leftarrow statements that the qubits (on the left hand) are converted or mapped to the quantum state (on the right hand), or the value (on the right hand) is stored in the variable (on the left hand).

Algorithm 1 Quantum Adders for Multiple Bits

Input: Two N-bit binary integers: $(a_{N-1}\cdots a_0)_{bin}, (b_{N-1}\cdots a_0)_{bin}.$ $A_{N-1},\cdots, A_0 \leftarrow |a_{N-1}\cdots a_0\rangle,$ $B_{N-1},\cdots, B_0, B_{-1} \leftarrow |b_{N-1}\cdots b_00\rangle,$ $C_N,\cdots, C_0 \leftarrow |0\cdots 0\rangle.$ $n \leftarrow 0$ while n < N do do \hat{P}_I or \hat{P}_{II} on $A_n, B_n, C_n, C_{n+1}, C_{n+2},$ $C_n \leftarrow |s_n\rangle, C_{n+1} \leftarrow |c_n^{out}\rangle.$ do $n \leftarrow n+1$ end while Output: $C_N, \cdots, C_0 \leftarrow |s_N \cdots s_0\rangle.$

We denote the quantum adder in Alg.(1) as $P_I(A_{N-1}, \dots, A_0; C_N, \dots, C_0; B_{N-1}, \dots, B_0)$ and $P_{II}(A_{N-1}, \dots, A_0; B_{N-1}, \dots, B_0; C_N, \dots, C_0)$, where the subscripts refer to the first type or second type quantum adder as shown in Eq.(6,7). For simplicity, the involved qubits, and the corresponding quantum states, are given from left columns to right columns, from top to bottom, as depicted in Fig.(2c,d). We have

$$P_{I}|a_{N-1}\cdots a_{0}, 0\cdots 0, b_{N-1}\cdots b_{0}\rangle$$

= $|a_{N-1}\cdots a_{0}, s_{N}\cdots s_{0}, b_{N-1}\cdots b_{0}\rangle$ (8)

and

$$P_{II}|a_{N-1}\cdots a_0, b_{N-1}\cdots b_0, 0\cdots 0\rangle = |a_{N-1}\cdots a_0, b_{N-1}\cdots b_0, s_N\cdots s_0\rangle$$
(9)

where for simplicity, the involved qubits are omitted, and the notation of quantum adders are abbreviated as P_I , P_{II} .

To add the two N-bit binary integers, the quantum one-bit full adder is applied N times, and the full quantum circuit can be decomposed into $\mathcal{O}(N)$ one-qubit or CNOT gates. The proposed quantum adder supporting multi-bit addition works like the typical ripple-carry adder, where each carry bit "ripples" to the next full adder. Thus, we have to repeat the quantum one-bit full adders step by step, and the time complexity is also $\mathcal{O}(N)$, and the circuit depth is of the same order.

C. Special Quantum Adders Supporting Multiple Bits

In Sec.(IIB) we present two types of quantum adders that support multiple bits. These two quantum adders are both feasible implementations of the binary addition as described in Eq.(1,2). Even though, these quantum adders can be 'expensive' in more intricate arithmetic logic circuits, especially for iterative additions. Recalling Fig.(2c,d), the states of qubits A, B that correspond to the input integers do not change after applying the full circuit, and the outputs correspond to the final state of qubits C, which are initialized at state $|0\rangle$ at the beginning. Thus, every time we add two N-bit binary integers, N+1 qubits are required to store the output. In intricate arithmetic logic circuits, such as multipliers and dividers as discussed in Sec.(IV) and Sec.(V), there are often iterative additions, and it is hardly affordable to assign additional qubits to store the temporary outputs of the iterative additions.

To address this issue, in this section we propose a special quantum adder, where no additional qubits are required to store the output. For simplicity, the special quantum adder is denoted as P_{III} , referring to the third type quantum adder proposed in this paper. In Fig.(5a) we present the required qubits and their connectivity for P_{III} . The inputs are two N bit integers $(a_{N-1}\cdots a_0)_{bin}, (b_{N-1}\cdots b_0)_{bin},$ mapped to 2N qubits denoted as A_{N-1}, \cdots, A_0 and B_{N-1}, \cdots, B_0 . We need one more qubit B_N to store the outputs, as the final output is a N + 1-bit binary integer. Qubits B_N, \dots, B_0 will be converted to state $|s_N, \dots, s_0\rangle$ at end, indicating the output sum $(s_N \cdots s_0)_{bin}$. Additionally, there are N+1 ancilla qubits denoted as C_{N-1}, \cdots, C_0 . These qubits are initialized at $|0\rangle$, and will still be at state $|0\rangle$ by the end. Thus, we can still use these ancilla qubits in the succeeding addition operations.

There are two main tasks in the implementation of P_{III} . One task is to calculate the output carry and the output sum. The other is to reset the ancilla qubits to state $|0\rangle$. As depicted in Fig.(6), we present the key operations in P_{III} , denoted as U_C and U_S , where the subscripts indicate the output carry (C) and the output sum (S). U_C is designed to work as Eq.(4). The operations before ϕ_{IV} is exactly the same to P_{II} , as depicted in Fig.(4). After ϕ_{IV} , the first three CNOT gates realize operation $X^{a\oplus b}$ on qubit C_{n+1} , and the other two CNOT gates are included to reset qubit A_n and B_n to state $|a\rangle$ and $|b\rangle$. Therefore we have

$$U_{C}(A_{n}, B_{n}, C_{n+2}, C_{n+1}, C_{n})|a_{n}, b_{n}, 0, 0, c_{in}^{n}\rangle$$

= $|a_{n}, b_{n}, 0, c_{in}^{n+1}, c_{in}^{n}\rangle$ (10)

where the output carry of the n^{th} bit c_{out}^n is also the input carry of the $(n + 1)^{th}$ bit c_{in}^{n+1} . Notice that U_C is reversible, we can reset qubit C_{n+1} to $|0\rangle$ by applying U_C^{\dagger} , as

$$U_{C}^{\dagger}(A_{n}, B_{n}, C_{n+2}, C_{n+1}, C_{n})|a_{n}, b_{n}, 0, c_{in}^{n+1}, c_{in}^{n}\rangle = |a_{n}, b_{n}, 0, 0, c_{in}^{n}\rangle$$
(11)

As for U_S , it works as Eq.(3), and we have

$$U_S(A_n, B_n, C_n) | a_n, b_n, c_{in}^n \rangle = | a_n, s_n, c_{in}^n \rangle \quad (12)$$

Algorithm 2 Quantum Adder P_{III}

Input: Two N-bit binary integers: $(a_{N-1}\cdots a_0)_{bin}, (b_{N-1}\cdots a_0)_{bin}.$ $A_{N-1}, \cdots, A_0 \leftarrow |a_{N-1} \cdots a_0\rangle,$ $B_N, B_{N-1}, \cdots, B_0 \leftarrow |0b_{N-1} \cdots b_0\rangle,$ $C_N, \cdots, C_0 \leftarrow |0 \cdots 0\rangle.$ $n \leftarrow 0$ while n < N do do U_C on $A_n, B_n, C_n, C_{n+1}, C_{n+2},$ $C_n \leftarrow |s_n\rangle, C_{n+1} \leftarrow |c_n^{out}\rangle.$ do $n \leftarrow n+1$ end while do SWAP on $B_N, C_N,$ $B_N \leftarrow |s_N\rangle, C_N \leftarrow |0\rangle.$ $n \leftarrow N-1$ while n > 0 do do U_S on $A_n, B_n, C_n,$ $B_n \leftarrow |s_n\rangle, C_n \leftarrow |0\rangle.$ do U_C^{\dagger} on $\check{A}_{n-1}, B_{n-1}, C_{n+1}, C_n, C_{n-1},$ $C_n \leftarrow |0\rangle.$ do $n \leftarrow n-1$ end while do CNOT on A_0, B_0 (A_0 is control qubit), $B_0 \leftarrow |s_0\rangle.$ **Output:** $B_N, \cdots, B_0 \leftarrow |s_N \cdots s_0\rangle$.

We present in Alg.(1) the algorithm to implement quantum adder P_{III} , which works as follows. The first step is to apply U_C for each digit, from LSB to MSB. The U_C operations prepare qubit C_n at state $|c_{in}^n\rangle$ $(n = 0, 1, \cdots, N)$, while qubits A_n and B_n are kept as the input state $|a_n\rangle$ and $|b_n\rangle$ $(n = 0, 1, \dots, N - 1)$, and B_N is still at state $|0\rangle$. Then apply a SWAP gate between qubits C_N and B_N , swapping the quantum states of these two qubits. Thus, B_N is converted to state $|c_{in}^N\rangle$, and C_N is reset to state $|0\rangle$. Notice that $|c_{in}^N\rangle$, or $|c_{out}^{N-1}\rangle$, is also the MSB of output sum, $|s_N\rangle$. By this mean, we have qubits C_N and B_N at the correct output states. In Fig.(5b) we present the activated qubits till this step. The activated qubits are marked with the light yellow background, where each square represents a physical qubit, corresponding to Fig.(5a). Hereafter, our aim is to convert qubits B_n and C_n $(n = 0, 1, \cdots, N - 1)$ to the correct output states. For each digit $(n = N - 1, N - 2, \dots, 1)$, from top to bottom), apply U_S on qubits A_n , B_n , and C_n , and then apply U_C^{\dagger} to qubits A_{n-1} , B_{n-1} , C_{n+1} , C_n and C_{n-1} . U_S converts qubit B_n to the correct output $|s_n\rangle$, while U_C^{\dagger} reset qubit C_n to state $|0\rangle$. By the end, for qubits A_0 , B_0 , C_0 that represent the LSB, we do not need to apply the full U_S . Instead, a single CNOT gate on qubits A_0 , B_0 (A_0 is control qubit) can convert B_0 to the correct output $|s_0\rangle$, as the input carry for the least



FIG. 5: (a) Required qubits and their connectivity for the special quantum adder, P_{III} . Squares in the graph represent physical qubits and edges are the allowed interactions. (b,c) Diagram of the activated qubits in P_{III} . The squares correspond to the qubits as depicted in (a), and the activated qubits are highlighted in light yellow.



FIG. 6: Detailed quantum circuits of operation U_C and U_S . The subscripts indicate the output carry (C) and the output sum (S). U_C computes the output carry, and the operations before ϕ_{IV} is exactly the same to P_{II} , as depicted in Fig.(4). U_S computes the output sum, formed by two CNOT gates.

significant bit is 0. The activated qubits are marked with the light yellow background in Fig.(5c). In brief, $P_{III}(A_{N-1}, \dots, A_0; B_N, \dots, B_0; C_N, \dots, C_0)$ works as

$$\begin{array}{l}
P_{III}|a_{N-1}\cdots a_0, 0b_{N-1}\cdots b_0, 0\cdots 0\rangle \\
= |a_{N-1}\cdots a_0, s_N s_{N-1}\cdots s_0, 0\cdots 0\rangle
\end{array}$$
(13)

where the involved qubits of P_{III} are omitted for simplicity.

There are 23 CNOT gates and 3 $C\sqrt{X}$ gates in the decomposition of U_C , and 2 CNOT gates in U_S . In the quantum adder P_{III} that adds two N-bit integers, U_C is applied N times, U_C^{\dagger} is also applied N times, and U_S is applied N - 1 times. Moreover, there is a SWAP gate between qubits B_N and C_N (can be decomposed as 2 CNOT gates, as one qubit is at $|0\rangle$ initially), and one single CNOT gate between A_0 and C_0 . In total, P_{III} of two N-bit integers can be decomposed into $\mathcal{O}(N)$ two-qubit gates. As these operations can not run in parallel, the time complexity is also of the order $\mathcal{O}(N)$.

Notice that in P_{III} , the two given terms are not equivalent. The special quantum adder does not change one input denoted as $(a_{N-1}\cdots a_0)_{bin}$. On the contrary, $(b_{N-1}\cdots b_0)_{bin}$ is replaced by the output sum. To calculate a succession of additions, it is convenient to map the new terms to column A, and use column B to store the temporary results.

III. TWO'S COMPLEMENT AND QUANTUM SUBTRACTOR

Two's complement is the most common method of representing signed (positive, negative, and zero) integers in classical computers or processors[26, 27]. In two's complement representation, the value ω of a N + 1 bit integer $(a_N, a_{N-1} \cdots a_0)_{bin}$ is given as

$$\omega = -2^N a_N + \sum_{j=0}^{N-1} 2^j a_j \tag{14}$$

where a_N is sign bit indicating the sign, $a_N = 0$ for non-negative and $a_N = 1$ for negative integer. The two's complement representation of a nonnegative number is just its ordinary binary representation, with sign bit 0. The two's complement representation of a negative binary number can be obtained by two steps: Firstly all bits are inverted, or "flipped", and the value of 1 is then added to the resulting value, ignoring the overflow (which occurs when taking the two's complement of 0). Recently, a variety of quantum approaches have been proposed to compute the two's complement representation on quantum computers [72, 73]. Even though, it is still challenging to implement these circuits on near-term quantum computers, mainly due to the required two- or multi-qubit gates among remote qubits. In this section, we present a feasible quantum circuits that calculates the two's complement of a given signed integer. Moreover, we then demonstrate how to use the method of two's complement to implement subtraction on quantum adders. Similar to the quantum adders as discussed in Sec.(II), the proposed circuits utilize only Pauli-X gates, CNOT gates, and $C\sqrt{X}$ (CSX) gates, and all two-qubit gates are operated between nearest neighbor qubits. Therefore, it is feasible to implement these operations on near-term quantum computers, where qubits are arranged in two-dimensional arrays.

A. Obtain the Two's Complement of A Negative Integer

Hereafter we present the quantum operation that generates the two's complement representation of a given negative integer. The input is a N + 1bit binary string, $a_N a_{N-1} \cdots a_0$, where the sign bit $a_N = 1$ indicates that it is negative, and $(a_{N-1} \cdots a_0)_{bin}$ is the absolute binary representation of the given integer. The inputs are mapped to N + 1 qubits A_N, \cdots, A_0 as $|a_N a_{N-1} \cdots a_0\rangle$. Our aim is to convert the inputs into the correct output state $|\tilde{a}_N \tilde{a}_{N-1} \cdots \tilde{a}_0\rangle$, where $(\tilde{a}_N, \tilde{a}_{N-1} \cdots \tilde{a}_0)$ is the two's complement representation, the sign bit is still $\tilde{a}_N = 1$. Recalling Eq.(14), we have

$$-2^{N} + \sum_{j=0}^{N-1} 2^{j} \tilde{a}_{j} = -\sum_{j=0}^{N-1} 2^{j} a_{j}$$
(15)

Similar to the procedure on classical computers, there are mainly two steps to obtain $|\tilde{a}_N \tilde{a}_{N-1} \cdots \tilde{a}_0\rangle$. The first step is to invert all bits of the absolute, $a_{N-1} \cdots a_0$. The second step is to add 1 to the entire inverted number, ignoring any overflow. The first step can be implemented by NPauli-X gates acting on qubits A_{N-1}, \cdots, A_0 , which convert these qubits to state $|\bar{a}_{N-1} \cdots \bar{a}_0\rangle$, where

$$|\bar{a}_n\rangle = X|a_n\rangle, \qquad n = 0, 1, \dots N - 1$$
 (16)

The second step, theoretically, can be implemented by P_{II} or P_{III} , where 1 is treated as one term in addition. Notice that in the *N*-bit representation of 1, all bits except the LSB is 0, which enables us to implement the second step using a shallower circuit instead of directly applying P_{II} or P_{III} . For simplicity, we denote the quantum operation that calculates the sum of $(\bar{a}_{N-1}\cdots \bar{a}_0)_{bin}$ and 1 as P_{+1} , where the input is a *N*-bit binary integer denoted as $(\bar{a}_{N-1}\cdots \bar{a}_0)_{bin}$.

Recalling the implementation of P_{II} or P_{III} in Sec.(II), there are 3 inputs for each digit except the LSB, the input carry and two bits from the input integers. In P_{+1} , however, there are always 2 inputs for each digit. For LSB, the inputs are 1 and b_0 . For the n^{th} digits $(n = 1, 2, \dots N - 1)$, the inputs are the input carry \tilde{c}_{in}^n and \bar{a}_n . Thus, we do not need to apply the quantum one-bit full adder. For each digit, P_{+1} acts the addition as

$$\tilde{a}_n = \tilde{c}_{in} \oplus \bar{a}_n \tag{17}$$

$$\tilde{c}_{out}^n = \tilde{c}_{in}^n \cdot \bar{a}_n \tag{18}$$

where the sum is denoted as \tilde{a} , and the carry is denoted as \tilde{c} to avoid confusions with Eq.(1,2). The output sum $(\tilde{a}_N \cdots \tilde{a}_0)_{bin}$ is a N+1-bit integer, and

$$(\tilde{a}_N \cdots \tilde{a}_0)_{bin} = (\bar{a}_{N-1} \cdots \bar{a}_0)_{bin} + 1$$
 (19)

where the MSB \tilde{a}_N represents the overflow of the addition. For clarity, here we study the simpler case, including the overflow. Later will give the operation that ignoring the overflow, which is integral to obtain the two's complement representation.

Recalling the implementation of P_{III} , P_{+1} can be treated as a special formation of P_{III} , where one input integer is always 1. Similarly, we can rewrite the addition of P_{+1} in the context of quantum,

$$|\tilde{a}_n\rangle = X^{\tilde{c}_{in}^n} |\bar{a}_n\rangle \tag{20}$$

$$|\tilde{c}_{out}^n\rangle = X^{\frac{3}{2}(\bar{a}_n \oplus \tilde{c}_{in}^n) + \frac{1}{2}(\bar{a}_n + \tilde{c}_{in}^n)}$$
(21)

These operations can be implemented by a chain of special quantum 'one-bit' adders, which works like classical half adders. Consider 4 qubits A_n, C_n , C_{n+1}, C_{n+2} as depicted in Fig.(8b). A_n is initialized at state $|\bar{a}_n\rangle$, C_n is initialized at $|\tilde{c}_{in}^n\rangle$, C_{n+1} , C_{n+2} are initialized at state $|0\rangle$. Eq.(20) can be implemented by a CNOT gate. To implement Eq.(21), we develop an operation U_C as depicted in Fig.(7). The first part of \tilde{U}_C corresponds to operation $X^{\frac{1}{2}\tilde{a}_n}$. As depicted in Fig.(7), the operations before the dashed line ϕ'_I converts qubit C_{n+2} to state $X^{\frac{1}{2}\tilde{a_n}}|0\rangle$, and then next two CNOT gates are applied between ϕ'_{I} and ϕ'_{II} , swapping the states of qubit C_{n+1} and qubit C_{n+2} . The succeeding $C\sqrt{X}$ gate corresponds to operation $X^{\frac{1}{2}\tilde{c}_{in}^n}$. By the end, the operations after ϕ'_{III} correspond to operation $X^{\frac{3}{2}(\bar{a}_n \oplus \tilde{c}^n_{in})}$. Notice that CNOT gates and $C\sqrt{X}$ gates commute, the operation $CX^{\frac{3}{2}}$ can be implemented by a CNOT gate along with a $C\sqrt{X}$ gate. U_C works as follows,

$$\hat{U}_C(A_n, C_n, C_{n+1}, C_{n+2}) | \bar{a}_n, \tilde{c}_{in}^n, 0, 0 \rangle$$

$$= | \bar{a}_n, \tilde{a}_n, \tilde{c}_{in}^{n+1}, 0 \rangle$$

$$(22)$$

where \tilde{a}_n and \tilde{c}_n are given in Eq.(17) and Eq.(18).

Hereafter we demonstrate the implementation of operation P_{+1} , which is constituted by a cascade of U_C and CNOT gates. Initially, N qubits A_n (n = $(0, 1, \dots, N-1)$ is prepared at state $|\bar{a}_n\rangle$, corresponding to the input N-bit integer $(0a_{N-1}\cdots a_0)_{bin}$. There is one additional qubit A_N , which is prepared at $|0\rangle$, and will store the overflow of the final output. The N + 2 ancilla qubits C_n $(n = 0, 1, \dots, N + 1)$ are all initialized at $|0\rangle$. Firstly, Pauli-X gate is applied on qubit C_0 , generating the one-bit integer 1 in the addition. Then apply U_C from LSB (corresponding to qubits A_0, C_2, C_1, C_0 to MSB (qubits $A_{N-1}, C_{N+1}, C_N, C_{N-1}$). By this mean, we have all qubits C_n at state $|\tilde{c}_{in}^n\rangle$ $(n = 0, \dots, N)$, corresponding to the input carry \tilde{c}_{in}^n . Next, apply a SWAP gate between C_N and A_N . Thus, we have qubit A_N at state $|\tilde{c}_{in}^N\rangle$, which is also the MSB of the output sum, and can be rewritten as $|\tilde{a}_N\rangle$. Meanwhile, ancilla qubit C_N is reset to $|0\rangle$. Iteratively, apply CNOT gates (qubits C are control qubits) and \tilde{U}_C^{\dagger} from MSB to the second least significant bit. By this mean, we have prepared qubit A_n at state $|\tilde{a}_n\rangle$, and reset ancilla qubit C_n at state $|0\rangle$ $(n = N-1, \cdots, 1)$. As for the LSB, a CNOT gate is applied on C_0 and A_0 , where C_0 is the control qubit. The CNOT gate converts A_0 to state $|\tilde{a}_0\rangle$, corresponding to the LSB of output sum. By the end, a Pauli-X gate is applied on qubit C_0 , resetting it to state $|0\rangle$. In Fig.(8c,d), the activated qubits in the above steps are highlighted with light yellow background, and the applied operations are marked at top.

We present in Alg.(3) the algorithm to implement quantum operation P_{+1} . In brief,

$$P_{+1}(A_N, \cdots, A_0; C_{N+1}, \cdots, C_0) \text{ works as}$$

$$P_{+1} |0\bar{a}_{N-1} \cdots \bar{a}_0, 0 \cdots 0\rangle$$

$$= |\tilde{a}_N \cdots \tilde{a}_0, 0 \cdots 0\rangle$$
(23)

where the involved qubits of P_{+1} are omitted for simplicity.

Notice that P_{+1} takes the account of the overflow. However, to obtain the two's complement of a negative integer, we need to add 1 to the inverted integer, ignoring any overflow. In Alg.(4) we present the algorithm to implement quantum operation P_{+1} , where the overflow is ignored. In $\tilde{P}_{\pm 1}$, the operations generating \tilde{a}_N are deleted, comparing to the original version P_{+1} . As the overflow is ignored, we do not need to apply \tilde{U}_C on qubits $A_{N-1}, C_{N+1}, C_N, C_{N-1}$, nor the SWAP gate between C_N and A_N . In fact, qubits A_N and C_{N+1} are not required in \tilde{P}_{+1} . The activated qubits in each step of P_{+1} still correspond to the highlighted squares in Fig.(8c,d), except the ones in the dashed boxes (these operations can be deleted in P_{+1} , as the overflow is ignored). \tilde{P}_{+1} still converts the input integer to the sum, yet in the final output quantum state, the overflow digit is not included, and we have

$$P_{+1}|\bar{a}_{N-1}\cdots\bar{a}_0,0\cdots0\rangle$$

$$=|\tilde{a}_{N-1}\cdots\tilde{a}_0,0\cdots0\rangle$$

$$(24)$$

where $\bar{a}_{N-1} \cdots \bar{a}_0$ and $\tilde{a}_{N-1} \cdots \tilde{a}_0$ correspond to the input integer and output sum in Eq.(19).

In the decomposition of P_{+1} , \tilde{U}_C is applied N times. Additionally, there is N-1 CNOT gates, 2 Pauli-X gates and one SWAP gate (can be decomposed into two SWAP gates, as one input qubit is at $|0\rangle$). Totally, P_{+1} can be decomposed into $\mathcal{O}(N)$ two-qubit gates, along with 2 Pauli-X gates. These operations are applied step by step instead of in parallel. Therefore, the overall time complexity of P_{+1} is $\mathcal{O}(N)$. Similarly, the time complexity of \tilde{P}_{+1} is also $\mathcal{O}(N)$.

Herein we can give the procedure to obtain the two's complement representation of a given negative integer. The input is a Nbit integer $(a_{N-1}\cdots a_0)_{bin}$, mapped to N qubits There are N + 2 ancilla qubits $A_{N-1},\cdots,A_0.$ C_{N+1}, \cdots, C_0 . Additionally, we need one more qubit denoted as A_N , which indicates the sign of the output binary integer. The connectivity of these 2Nqubits are as depicted in Fig. (8a), where C_{N+1} is not necessary. At beginning, A_{N-1}, \dots, A_0 are initialized at state $|a_N \cdots a_0\rangle$, whereas $A_N, C_{N+1}, \cdots, C_0$ are all initialized at state $|0\rangle$. The two's complement representation can be obtained in two steps. Firstly, apply Pauli-X gate on qubits A_N, \dots, A_0 . Next, apply P_{+1} on qubits A_N, \dots, A_0 , and C_{N+1}, \dots, C_0 . These two steps corresponds to the classical approach to obtain the two's complement representation. The first step 'flips' each bit, and the sign bit is



FIG. 7: Detailed quantum circuits of operation \tilde{U}_C . Four qubits are involved in \tilde{U}_C . Qubit A_n is initialized at state $|\bar{a}_n\rangle$, corresponding to the input, whereas qubit C_n is initialized at state $|\tilde{c}_{in}^n\rangle$, representing the input carry. States of qubits A_n , C_n do not change after applying \tilde{U}_C . Qubit C_{n+1} is initialized at state $|0\rangle$, and is converted to state $|\tilde{c}_{in}^{n+1}\rangle$ (or equivalently, $|\tilde{c}_{out}^n\rangle$) by the end, corresponding to the output carry. Qubit C_{n+2} is ancilla qubit, which is initialized at $|0\rangle$, and is reset at $|0\rangle$ after applying \tilde{U}_C . The operation $CX^{\frac{3}{2}}$ can be implemented by a CNOT gate along with a $C\sqrt{X}$ gate.



FIG. 8: (a) Required qubits and their connectivity for the special quantum adder, P_{+1} (\tilde{P}_{+1}). Squares in the graph represent physical qubits and edges are the allowed interactions. (b) Required qubits and their connectivity for operation \tilde{U}_C . (c,d) Diagram of the activated qubits in P_{+1} . The squares correspond to the qubits as depicted in (a), and the activated qubits are highlighted in light yellow.

also set as 1. The second step add 1 to the inverted integer, ignoring the overflow. At the end, we have qubits A_N, \dots, A_0 at state $|\tilde{a}_N \tilde{a}_{N-1} \cdots \tilde{a}_0\rangle$, where \tilde{a} is given as Eq.(15), and the MSB $\tilde{a}_N = 1$ indicates that the integer is negative. Meanwhile, the ancilla qubits C_{N+1}, \dots, C_0 are still at state $|0\rangle$. As for the time complexity, the Pauli-X gate is applied for Ntimes, and \tilde{P}_{+1} is applied once. In total, the time complexity is $\mathcal{O}(N)$. quantum subtractors, as discussed in Sec.(III B). Moreover, later in Sec.(III C), we will show that \tilde{P}_{+1} is integral in the operation that computes the two's complement representation of arbitrary signed integers, where the initializing process is replaced (The replaced lines are noted with * and ** in Alg.(4).

 ${\cal P}_{+1}$ is a key operation in the implementation of

Algorithm 3 Operation P_{+1} , overflow included

Input: One N-bit binary integers: $(a_{N-1}\cdots a_0)_{bin}.$ $A_N, \cdots, A_0 \leftarrow |0a_{N-1}\cdots a_0\rangle,$ $C_{N+1}, \cdots, C_0 \leftarrow |0 \cdots 0\rangle.$ do Pauli-X gate on C_0 , $C_0 \leftarrow |1\rangle.$ $n \leftarrow 0$. while n < N do do \tilde{U}_C on $A_n, C_{n+2}, C_{n+1}, C_n,$ $C_{n+1} \leftarrow |\tilde{c}_{in}^{n+1}\rangle.$ do $n \leftarrow n+1$ end while do SWAP gate on A_N , C_N , $A_N \leftarrow |\tilde{a}_N\rangle, C_N \leftarrow |0\rangle.$ $n \gets N-1$ while n > 0 do do CNOT gate on A_n, C_n (C_n is control qubit), $A_n \leftarrow |\tilde{a}_n\rangle.$ do \tilde{U}_C^{\dagger} on $\tilde{A}_{n-1}, C_{n+1}, C_n, C_{n-1},$ $C_n \leftarrow |0\rangle.$ $\mathbf{do}\ n \leftarrow n-1$ end while do CNOT on A_0, C_0 (C_0 is control qubit), $A_0 \leftarrow |\tilde{a}_0\rangle.$ do Pauli-X gate on C_0 , $C_0 \leftarrow |0\rangle.$ **Output:** $A_N, \cdots, A_0 \leftarrow |\tilde{a}_N \cdots \tilde{a}_0\rangle$.

B. Implement Subtraction with Quantum Adder

Classical computers usually use the method of complements to implement subtraction with adders. Denote $(d_N \cdots d_0)_{bin}$ as the difference of minuend $(a_{N-1} \cdots a_0)_{bin}$ and subtrahend $(b_{N-1} \cdots b_0)_{bin}$,

$$(d_N \cdots d_0)_{bin} = (a_{N-1} \cdots a_0)_{bin} - (b_{N-1} \cdots b_0)_{bin}$$
(25)

where $(a_{N-1}\cdots a_0)_{bin}$ and $(b_{N-1}\cdots b_0)_{bin}$ are two N-bit non-negative integers without sign bit. On the contrast, $(d_N \cdots d_0)_{bin}$ is given in the two's complement representation. The sign bit $d_N = 1$ if the difference is negative, whereas $d_N = 0$ if the difference is non-negative. Recalling the definition of two's complement representation, we have

$$-2^{N}d_{N} + \sum_{j=0}^{N-1} 2^{j}d_{j} = \sum_{j=0}^{N-1} 2^{j}a_{j} + \sum_{j=0}^{N-1} 2^{j}\tilde{b}_{j} - 2^{N}\tilde{b}_{N}$$
(26)

where $(\tilde{b}_N \tilde{b}_{N-1} \cdots \tilde{b}_0)_{bin}$ is the two's complement representation of $(-b_{N-1} \cdots b_0)_{bin}$. By this mean, the subtraction is converted to addition.

Algorithm 4 Operation \tilde{P}_{+1} , overflow ignored

Input: One N-bit binary integer: $(a_{N-1}\cdots a_0)_{bin}$. $A_N, \cdots, A_0 \leftarrow |0a_{N-1} \cdots a_0\rangle,$ $C_{N+1}, \cdots, C_0 \leftarrow |0 \cdots 0\rangle.$ * do Pauli-X gate on C_0 , $C_0 \leftarrow |1\rangle.$ $n \leftarrow 0$. while n < N - 1 do do \tilde{U}_C on $\begin{array}{l} A_n, C_{n+2}, C_{n+1}, C_n, \\ C_{n+1} \leftarrow |\tilde{c}_{in}^{n+1}\rangle. \end{array}$ do $n \leftarrow n+1$ end while $n \leftarrow N - 1$ while n > 0 do do CNOT gate on A_n, C_n (C_n is control qubit), $A_n \leftarrow |\tilde{a}_n\rangle.$ do \tilde{U}_C^{\dagger} on $A_{n-1}, C_{n+1}, C_n, C_{n-1},$ $C_n \leftarrow |0\rangle.$ do $n \leftarrow n-1$ end while do CNOT on A_0, C_0 (C_0 is control qubit), $A_0 \leftarrow |\tilde{a}_0\rangle.$ ** do Pauli-X gate on C_0 , $C_0 \leftarrow |0\rangle.$ **Output:** $A_{N-1}, \cdots, A_0 \leftarrow |\tilde{a}_{N-1} \cdots \tilde{a}_0\rangle$.

Similarly, it is feasible to calculate subtraction with quantum adder. Consider 3N + 3 qubits $A_{N-1}, \dots, A_0, B_N, \dots, B_0, C_{N+1}, \dots, C_0$. The connectivity is as depicted in Fig.(5) (qubit C_{N+1} connects to C_N , qubit C_{N+1} is not included in Fig.(5)). The inputs are two N-bit integers $(a_{N-1} \cdots a_0)_{bin}$ and $(b_{N-1} \cdots b_0)_{bin}$, and our aim is to obtain the difference $(d_N \cdots d_0)_{bin}$ as given in Eq.(25). Initially, qubits A_{N-1}, \dots, A_0 are prepared at $|a_{N-1} \cdots a_0\rangle$, qubits B_{N-1}, \dots, B_0 are prepared at $|b_{N-1} \cdots b_0\rangle$, and qubits B_N, C_N, \dots, C_0 are prepared at $|0\rangle$.

The first step is to prepare the two's complement representation of $(-b_{N-1}\cdots b_0)_{bin}$. As discussed in Sec.(III A), we can apply Pauli-X gates on each qubit B, and then apply \tilde{P}_{+1} on qubits B_N, \cdots, B_0 , and C_{N+1}, \cdots, C_0 . Then we have qubits B_N, \cdots, B_0 at state $|\tilde{b}_N \tilde{b}_{N-1} \cdots \tilde{b}_0\rangle$, corresponds to the two's complement representation of $(-b_{N-1}\cdots b_0)_{bin}$.

Next, apply P_{II} on qubits A_{N-1}, \dots, A_0 , $B_{N-1}, \dots, B_0, C_N, \dots, C_0$. Notice that the sign bit B_N is not included in this step. $|a_{N-1} \cdots a_0\rangle$ and $|\tilde{b}_{N-1} \cdots \tilde{b}_0\rangle$ are treated as two input terms in the addition, and the output is stored in qubits $C_N, \cdots, C_0.$

Finally, apply CNOT gate on B_N and C_N , where B_N is the control qubit. By this mean, we have qubits C_N, \dots, C_0 at state $|d_N \dots d_0\rangle$, where $(d_N \dots d_0)_{bin}$ is the difference in two's complement representation, and d_N is the sign bit.

According to Sec.(III A), the time complexity to obtain the two's complement representation is $\mathcal{O}(N)$. The time complexity of P_{II} is also $\mathcal{O}(N)$. Thus, the total time complexity of this quantum subtractor is also $\mathcal{O}(N)$.

Sometimes we need to sum up the input signed integers iteratively, where one input is always negative and the other is not. For example, in quantum multiplier and quantum divider as presented later in Sec.(IV) and Sec.(V), we iteratively calculate the contribution for each digit, where we need to add up the temporary results (signed, can be negative) along with the temporary sums. In this cases, it is hardly wisdom to apply the quantum subtractor based on P_{II} , as it is too expensive to assign qubits to store these temporary sums. To address this issue, in Alg.(5), we present the quantum adder for signed integers, which is denoted as \tilde{P}_{III} . There are two signed integers as input, $(a_{N-1}, a_{N-2} \cdots a_0)_{bin}$, and $(b_{N-1}, b_{N-2} \cdots b_0)_{bin}$, where a_{N-1}, b_{N-1} are sign bits, and the integers are already given in the two's complement representation. The required connectivity is as depicted in Fig.(5a), where qubit B_N is not necessary. The given signed integers are mapped to qubits $A_{N-1}, \cdots, A_0, B_{N-1}, \cdots, B_0$, where the outputs are also stored in B_{N-1}, \cdots, B_0 . P_{III} works like P_{III} , but ignoring the overflow. The output is also a signed integer in the two's complement representation. The time complexity of P_{III} is also $\mathcal{O}(N)$.

At the end of this subsection, we will demonstrate a useful feature of the operation \tilde{P}_{III} . For an arbitrary non-negative binary integer $(a_{N-1}\cdots a_0)_{bin}$, we have

$$(0, a_{N-1} \cdots a_0)_{bin} + (1, \tilde{a}_{N-1} \cdots \tilde{a}_0)_{bin}$$

=(1, 0, 0 \cdots 0)_{bin} (27)

where $(1, \tilde{a}_{N-1} \cdots \tilde{a}_0)_{bin}$ is the two's complement representation of $(-a_{N-1} \cdots a_0)_{bin}$. In the summation, all digits are 0, except the first 1 which is an overflow. For the quantum adder P_{III} , we have

$$P_{III}|0a_{N-1}\cdots a_0, 01\tilde{a}_{N-1}\cdots \tilde{a}_0, 0\cdots 0\rangle$$

= $|0a_{N-1}\cdots a_0, 100\cdots 0, 0\cdots 0\rangle$ (28)

where in the second input term, $01\tilde{a}_{N-1}\cdots\tilde{a}_0$, the first digit 0 is a 'blank' to store the overflow, and the second digit 1 is the sign bit. As for the quantum adder \tilde{P}_{III} , we have

$$P_{III}|0a_{N-1}\cdots a_0, 1\tilde{a}_{N-1}\cdots \tilde{a}_0, 0\cdots 0\rangle$$

=|0a_{N-1}\cdots a_0, 00\cdots 0, 0\cdots 0\rangle (29)

Algorithm 5 Adder \tilde{P}_{III} for signed integers

Input: Two signed N-digit binary integers (in two's complement representation): $A_{N-1}, \cdots, A_0 \leftarrow |a_{N-1}, a_{N-2} \cdots a_0\rangle,$ $B_{N-1}, \cdots, B_0 \leftarrow |b_{N-1}, b_{N-2} \cdots b_0\rangle,$ $C_N, \cdots, C_0 \leftarrow |0 \cdots 0\rangle.$ $n \leftarrow 0$ while n < N - 1 do do U_C on $\begin{array}{l}
A_n, B_n, C_n, C_{n+1}, C_{n+2}, \\
C_n \leftarrow |s_n\rangle, C_{n+1} \leftarrow |c_{in}^{n+1}\rangle.
\end{array}$ do $n \leftarrow n+1$ end while do CNOT on C_{N-1} (Control), B_{N-1} (Target), **do** CNOT on A_{N-1} (Control), B_{N-1} (Target), $B_{N-1} \leftarrow |a_{N-1} \oplus b_{N-1} \oplus c_{in}^{N-1}\rangle$. do U_C^{\dagger} on $\tilde{A}_{N-2}, B_{N-2}, C_N, C_{N-1}, C_{N-2},$ $C_{N-1} \leftarrow |0\rangle.$ $n \leftarrow N-2$ while n > 0 do do U_S on $A_n, B_n, C_n,$ $B_n \leftarrow |s_n\rangle, C_n \leftarrow |0\rangle.$ do U_C^{\dagger} on $\tilde{A}_{n-1}, B_{n-1}, C_{n+1}, C_n, C_{n-1},$ $C_n \leftarrow |0\rangle.$ do $n \leftarrow n-1$ end while do CNOT on A_0, B_0 (A_0 is control qubit), $B_0 \leftarrow |s_0\rangle.$ **Output:** $B_N, \dots, B_0 \leftarrow |s_N \dots s_0\rangle$.

As \tilde{P}_{III} ignores the overflow, the output is just 0. This feature is of great convenience in the implementation of quantum multiplier and divider, as discussed later in Sec.(IV) and Sec.(V).

C. Obtain the Two's Complement of An Arbitrary Signed Integer

In Sec.(III A), we present how to obtain the quantum state that corresponds to the two's complement of a given negative integer. In this subsection we focus on a more general case, where the input is an arbitrary signed integer, either negative or nonnegative.

Consider N + 1 qubits A_N, A_{N-1}, \dots, A_0 . Qubits A_{N-1}, \dots, A_0 are initialized at state $|a_{N-1} \cdots a_0\rangle$, corresponding to the absolute value $(a_{N-1} \cdots a_0)_{bin}$. Qubit A_N is initialized at state $|a_N\rangle$, where a_N is the sign bit, $a_N = 0$ if the input is non-negative, and $a_N = 1$ if the input is negative. Our aim is to design a unitary operation U_{\pm} , that converts qubits $A_N, A_{N-1}, \cdots, A_0$ to state $|\tilde{a}_N \tilde{a}_{N-1}, \cdots, \tilde{a}_0\rangle$, where

 $\tilde{a}_N = a_N$ is still the sign bit. When the input is nonnegative, $a_N = 0$, U_{\pm} does not change anything, and we have $(\tilde{a}_{N-1}\cdots \tilde{a}_0)_{bin} = (a_{N-1}\cdots a_0)_{bin}$. On the contrary, for negative input $a_N = 1$, U_{\pm} converts qubits A_{N-1}, \cdots, A_0 to state $|\tilde{a}_{N-1}\cdots \tilde{a}_0\rangle$, where \tilde{a} is the two's complement representation of $(-a_{N-1}\cdots a_0)_{bin}$ as shown in Eq.(15).

Intuitively, U_{\pm} can be implemented by an intricate 'CU' operation, where the sign bit qubit A_N is the control qubit, and 'U' is the quantum operation that generates the two's complement representation of a given negative integer, as presented in Sec.(III A). However, due to the limitation of hardware, it is extremely challenging to implement such intricate 'CU' operation on near-term quantum computers.

To address this issue, hereafter we present a feasible operation denoted as U_{\pm} . Still, U_{\pm} can be implemented with only Pauli-X gates, CNOT gates, and $C\sqrt{X}$ (CSX) gates, and all two-qubit gates are operated between nearest neighbor qubits. U_{\pm} acts on 2N + 2 qubits. There are N + 1 qubits A_N, \dots, A_0 representing the given integer, where A_N is the sign bit. Additionally, we need N + 1ancilla qubits C_N, \dots, C_0 . These ancilla qubits are initialized at $|0\rangle$ at the very beginning. The connectivity of qubits A_N, \dots, A_0 and C_N, \dots, C_0 are as depicted in Fig.(8a) (ignoring C_{N+1}), where each square represents a physical qubit, and the edges indicate that the neighbor qubits are connected.

Recalling the quantum operation that generates the two's complement representation of a given negative integer, there are two main steps. Firstly, Pauli-X gates are applied on qubits A_{N-1}, \dots, A_0 , flipping these bits. Next, operation \tilde{P}_{+1} is applied, adding 1 to the inverted integer and ignoring the overflow.

For an arbitrary signed integer, the state of sign bit A_N is unknown. In the first step, our aim is to flip these bits if the input is negative, otherwise to do nothing. Here we apply operation U_{flip} to qubits $A_N, A_{N-1}, \cdots, A_0$ and ancilla qubit C_0 . The quantum circuit of U_{flip} is as depicted in Fig.(9a), and the activated qubits are assigned on the left side. Initially, qubits A_N, \dots, A_0 are prepared at input state $|a_N \cdots a_0\rangle$, while the ancilla qubit C_0 is at state $|0\rangle$. There are in total 2N + 1 CNOT gates, acting on the neighbor qubits that are physically connected. Notice that the quantum state of the control qubit does not change in a single CNOT gate. Thus, qubit A_N is always at state $|a_N\rangle$, indicating that U_{flip} does not change the sign bit. There is a CNOT gate connecting qubits A_N and A_{N-1} , where A_N is the control qubit. By applying the CNOT gate, qubit A_{N-1} is converted to state $X^{a_N}|a_{N-1}\rangle = |a_N \oplus a_{N-1}\rangle$. Then study the output state of A_{N-2} . There are two CNOT gates connecting A_{N-1} and A_{N-2} , where qubit A_{N-1} is always



FIG. 9: The implementation of U_{flip} and U_{res} . (a) U_{flip} flips a_{N-1}, \dots, a_0 for negative input $a_N = 1$, and meanwhile does nothing for non-negative input $a_N = 0$. (b) U_{res} resets the ancilla qubit to state $|0\rangle$.

the control qubit. When the first CNOT gate is applied, qubit A_{N-1} is at the initial state $|a_{N-1}\rangle$, whereas when the second one is applied, A_{N-1} is converted to state $|a_N \oplus a_{N-1}\rangle$. We have

$$X^{a_N \oplus a_{N-1}} X^{a_N-1} |a_{N-2}\rangle = |a_N \oplus a_{N-1} \oplus (a_N - 1 \oplus a_{N-2})\rangle$$
(30)
$$= |a_N \oplus a_{N-2}\rangle$$

Similarly, we have qubit A_n , $n = 0, 1, \dots, N-3$ converted to state $|a_N \oplus a_n\rangle$ by applying U_{flip} . As for the ancilla qubit C_0 , as it is initialized at $|0\rangle$, it is converted to output state $|a_N\rangle$. We have

$$U_{flip}(A_N, A_{N-1}, \cdots, A_0, C_0) | a_N, a_{N-1}, \cdots, a_0, 0 \rangle$$

= $|a_N, a_N \oplus a_{N-1}, \cdots, a_N \oplus a_0, a_N \rangle$
(31)

When the input is negative, $a_N = 1$, and the output $a_N \oplus a_n$ corresponds to the flipped bit. Otherwise, the input is non-negative, $a_N = 0$, and the output is still a_n . Therefore, U_{flip} flips the bits a_{N-1}, \dots, a_0 for negative input $a_N = 1$, and meanwhile does nothing for non-negative input $a_N = 0$.

The second step in generating the two's complement of a negative integer is adding 1 to the inverted integer, ignoring any overflow, which can be implemented by applying the operation \tilde{P}_{+1} . Here the given signed integer can be either negative or not, thus the original P_{+1} does not meet the requirement. Recalling the operation \tilde{P}_{+1} , the ancilla qubit C_0 is prepared at state $|0\rangle$ at beginning, then is fliped to state $|1\rangle$ (The line marked with * in Alg.(4)), corresponding to the term '1' in the addition. By the end, C_0 is reset to state $|0\rangle$ (The line marked with ** in Alg.(4)), as it is an ancilla qubit. For negative inputs $a_N = 1$, we still need to repeat these operations. Yet for non-negative inputs $a_N = 0$, we can leave C_0 at the initial state $|0\rangle$, then sum up $(a_{N-1}\cdots a_0)_{bin}$ and 0, and the output is still $(a_{N-1}\cdots a_0)_{bin}$. As shown in Eq.(31), U_{flip} also converts the ancilla qubit C_0 to state $|a_N\rangle$. Therefore, the second step can be implemented by applying P_{+1} without the lines marked with * and ** in Alg.(4). Notice that the ancilla qubit C_0 is still at state $|a_N\rangle$. Thus, we need to reset C_0 to state $|0\rangle$. As other ancilla qubits are all at state $|0\rangle$, we can apply U_{res} as depicted in Fig.(9b), where there are 2N + 1 CNOT gates.

In conclusion, the procedure of U_{\pm} can be given as follows:

0. Initially, a signed integer $(a_N a_{N-1} \cdots a_0)_{bin}$ is given, a_N is the sign bit, for negative input $a_N = 1$, otherwise $a_N = 0$. Qubits A_N, \cdots, A_0 are prepared at state $|a_N a_{N-1} \cdots a_0\rangle$, and ancilla qubits C_N, \cdots, C_0 are all prepared at state $|0\rangle$.

1. Firstly, apply operation U_{flip} to qubits A_N, \dots, A_0, C_0 . U_{flip} flips $a_N a_{N-1} \dots a_0$ if $a_N = 1$, as shown in Eq.(31).

2. Next, apply P_{+1} as shown in Alg.(4), ignoring the lines marked with * and **. By this mean, if $a_N = 1$ we add 1 to the inverted integer, ignoring overflow. Otherwise, we add 0 to the temporary results and nothing changes.

3. Finally, apply U_{res} on qubits A_N, C_N, \dots, C_0 , resetting the ancilla qubit C_0 to state $|0\rangle$.

 U_{\pm} works as follows,

$$U_{\pm}(A_N, \cdots, A_0; C_N, \cdots, C_0) |a_N a_{N-1} \cdots a_0, 0 \cdots 0\rangle$$

= $|a_N \tilde{a}_{N-1} \cdots \tilde{a}_0, 0 \cdots 0\rangle$ (32)

If $a_N = 1$, we have $\tilde{a}_n = \tilde{a}_n$, where \tilde{a}_n is given in Eq.(15). Otherwise $a_N = 0$, we have $\tilde{a}_n = a_n$, which is the original input. In conclusion, the two's complement representation \tilde{a} satisfies

$$-2^{N}a_{N} + \sum_{j=0}^{N-1} 2^{j}\tilde{a}_{j} = (1 - 2a_{N})\sum_{j=0}^{N-1} 2^{j}a_{j} \quad (33)$$

where a_N is the sign bit.

As the time complexity of U_{flip} , \tilde{P}_{+1} and U_{res} are all of the order $\mathcal{O}(N)$, we have the overall time complexity of U_{\pm} is also $\mathcal{O}(N)$. U_{\pm} plays an important role the in quantum multiplier and quantum divider, which is discussed in the following sections Sec.(IV) and Sec.(V).

IV. QUANTUM MULTIPLIER

Long multiplication is a natural way of multiplying numbers: multiply the multiplicand by each digit of the multiplier and then add up all the properly shifted results. Using long multiplication, the product of two unsigned binary integers $(a_{N-1}\cdots a_0)_{bin}$, $(b_{N-1}\cdots b_0)_{bin}$ can be calculated as

$$(a_{N-1}\cdots a_0)_{bin} \cdot (b_{N-1}\cdots b_0)_{bin} = \sum_{j=0}^{N-1} 2^j a_j \cdot (b_{N-1}\cdots b_0)_{bin}$$
(34)

Thus, the multiplication of two binary numbers comes down to several binary additions of the partial products.

Hereafter we present a design of quantum multiplier based on long multiplication.

The necessary qubits and their connectivity are as depicted in Fig.(10a), where the squares represent qubits, and the edges indicate that the nearest neighbor qubits are connected physically. There are 2N qubits, A_{N-1}, \dots, A_0 and B_{N-1}, \dots, B_0 , carrying the inputs $(a_{N-1}, \dots, a_0)_{bin}$ and $(b_{N-1}, \dots, b_0)_{bin}$. Additionally, an ancilla qubit, denoted as B_{-1} , is required. These 2N + 1 qubits are assigned in the second column (from left) as shown in Fig.(10a). Qubits A_{N-1}, \dots, A_0 are assigned at the top half, and then qubits $B_{N-1}, \cdots B_0$ at the bottom half, from top to bottom. The 2N + 2 qubits in the third column (from left) are denoted as C_{2N}, \cdots, C_{-1} , from top to bottom, which are designed to store the temporary results and the final outputs. Furthermore, 4N + 3 ancilla qubits, D_{2N-1}, \cdots, D_{-1} and E_{2N}, \dots, E_{-1} are necessary. As depicted in Fig.(10a), qubits D_{2N-1}, \dots, D_{-1} are assigned in the first column, and qubits E_{2N}, \dots, E_{-1} in the last column (from left). In total, there are 6N + 6qubits.

At beginning, qubits A_{N-1}, \dots, A_0 are initialized at state $|a_{N-1} \cdots a_0\rangle$, and $B_{N-1}, \dots B_0$ are initialized at $|b_{N-1} \cdots b_0\rangle$, corresponding to the input non-negative integers $(a_{N-1} \cdots a_0)_{bin}$ and $(b_{N-1} \cdots b_0)_{bin}$. The other qubits are all prepared at state $|0\rangle$.

According to Eq.(34), there are three main tasks in the long multiplication of each digit: calculating the partial product $a_j \cdot (b_{N-1} \cdots b_0)_{bin}$, shifting them, and sum up the shifted results. For binary inputs, if $a_j = 1$, the product $a_j \cdot (b_{N-1} \cdots b_0)_{bin}$ is just $(b_{N-1} \cdots b_0)_{bin}$, otherwise the product is 0. Intuitively, we can calculate the partial product using a quantum 'Controlled Adder', where qubit A_j is the control qubit. If qubit A_j is at state $|1\rangle$, the quantum adder works, summing up the properly shifted $(b_{N-1} \cdots b_0)_{bin}$ and the temporary results. However, it is of great difficulty to implement the



FIG. 10: The activated qubits in quantum multiplier. (a) The required qubits and connectivity for quantum multiplier. Each square represents a qubit, and the edges indicate that the neighbor are connected physically on a quantum computer. The inputs are mapped to qubits A and B in the second column (from left), whereas the temporary sums and the final output are stored in qubits C in the third column. Qubits D, E in the first and last columns are ancilla qubits. (b,c,d,e) The activated qubits in each step, where the activated qubits are highlighted in light blue. (b) The activated qubits in the first step, shifting the input integer $(b_{N-1} \cdots b_0)_{bin}$ to $\frac{1}{2}(b_{N-1} \cdots b_0)_{bin}$. (c) The activated qubits for partial product $a_0 \cdot (b_{N-1} \cdots b_0)_{bin}$. (d) The activated qubits for partial product $a_1 \cdot (b_{N-1} \cdots b_0)_{bin}$. (e) The activated qubits for partial product $a_{N-1} \cdot (b_{N-1} \cdots b_0)_{bin}$.

'Controlled Adder' on nowadays quantum computers (Toffoli gates among remote qubits are necessary in the implementation of such intricate operation, which can be decomposed into a series one-and two-qubit gates including considerable amounts of SWAP gates). Here we present an alternative solution to calcu-

late the partial product. Notice that

$$a_{j} \cdot (b_{N-1} \cdots b_{0})_{bin} = \frac{1}{2} (b_{N-1} \cdots b_{0})_{bin} + \frac{1}{2} (2a_{j} - 1)(b_{N-1} \cdots b_{0})_{bin}$$
(35)

where 1/2 indicates shifting. The first term in Eq.(35) is the input integer $(b_{N-1} \cdots b_0)_{bin}$. As for the other term, due to the binary input $a_j = 0, 1$, we have $2a_j - 1 = \pm 1$, which corresponds to the sign bit \bar{a}_j , where \bar{a}_j is the negation of a_j , also denoted as $\neg a_j$. For $a_j = 0$, we have $2a_j - 1 = -1$, meanwhile $\bar{a}_j = 1$ (For negative integer, the sign bit is 1 in two's complement representation, as discussed in Sec.(III A)). For $a_j = 1$, we have $2a_j - 1 = 1$, and $\bar{a}_i = 0$. In quantum computer, the Pauli-X gate conveniently converts state $|a_i\rangle$ into $|\bar{a}_i\rangle$. Thus, the partial product can be obtained by calculating two shifted parts, the original input $(b_{N-1} \cdots b_0)_{bin}$, and a signed integer $(\bar{a}_j, b_{N-1} \cdots b_0)_{bin}$. \bar{a}_j is the sign bit, $(b_{N-1}\cdots b_0)_{bin}$ is the absolute, where $\bar{a}_j = 1$ indicates negative. Recalling the discussions in Sec.(III A), we can apply U_{\pm} to prepare the two's complement representation of $(\bar{a}_j, b_{N-1} \cdots b_0)_{bin}$, and then apply the quantum adder to sum up the temporary results. By this mean, we can obtain the contribution of the second term in Eq.(35) on a quantum computer.

According to Eq.(34), the next task is to shift these partial products, and then sum up the temporary results. The shifting procedure can be implemented by moving the relative states up and down. As depicted in Fig.(10), qubits C_{2N}, \cdots, C_{-1} are assigned in the third column, designed to store the temporary sums and the final output. The subscript of qubit C_j indicates that its weight is 2^j , and qubits A_i (or B_i) and C_i in one row has the same weights. As a simple example, qubits $B_{N-1}, \cdots B_0$ are prepared at state $|b_{N-1}\cdots b_0\rangle$ initially, which represents the original integer $(b_{N-1} \cdots b_0)_{bin}$, as the LSB b_0 is mapped to qubit B_0 , whose weight is 2^0 . If we shift the inputs, and set qubits $B_{N-1}, \cdots B_{-1}$ at state $|b_{N-1\cdots b_0}\rangle$, then the state represents $\frac{1}{2}(b_{N-1}\cdots b_0)_{bin}$, as now the LSB b_0 is mapped to B_{-1} and the weight of B_{-1} is 2^{-1} . In this case, the whole state is moved down for one digit, corresponding to the shifting 2^{-1} (shift one bit to the right side). Similarly, the shifting 2^N (shift N bit to the right side) can be implemented by moving the whole quantum up for N digits. Thus, we can shift the partial product by moving the relative quantum states up and down.

We then need to sum up the shifted partial product (two terms) and the temporary sums, which can be implemented by P_{III} . The shifted partial product is one input term of P_{III} , assigned in the second column in Fig.(10). Another input of P_{III} , the temporary sum of the previous steps, is stored in the third column in Fig.(10). After applying P_{III} , the output is stored in the corresponding C qubits in the third column, which is the input temporary sum for the next digit. For each digit, from a_0 to a_{N-1} , repeat the procedures above, and at last the product can be obtained.

In Alg.(6) we present the algorithm for quantum multiplier based on long multiplication. Besides, to demonstrate the proposed quantum multiplier in a more detailed manner, we depict the activated qubits in each step as shown in Fig.(10b,c,d,e), where the activated qubits are colored in light blue. The tiny squares in Fig.(10b,c,d,e) corresponds to the squares in Fig.(10a).

The product is calculated based on long multiplication as shown in Eq.(34), from LSB a_0 to MSB a_{N-1} . After initialization, we have qubits B_{N-1}, \cdot, B_0 at state $|b_{N-1}\cdots b_0\rangle$, corresponding to the input non-negative integer $(b_{N-1}\cdots b_0)_{bin}$. Recalling Eq.(35), we can break the partial product into two parts with shifting 1/2. Thus, it is convenient to shift the input $(b_{N-1}\cdots b_0)_{bin}$. In Alg.(6), there are a series of CNOT gates in the first 'while' loop, which converts qubits $B_{N-1}, \cdot, B_0, B_{-1}$ to state $|0b_{N-1}\cdots b_0\rangle$. By this mean, we shift the original input $(b_{N-1}\cdots b_0)_{bin}$ to $\frac{1}{2}(b_{N-1}\cdots b_0)_{bin}$. In Fig.(10b), the activated qubits are highlighted in light blue. For clarity, we annotate the corresponding subscripts and weights in Fig.(10b).

In Fig.(10c), the activated qubits are highlighted in light blue, which are involved in the calculation of the partial product $a_0 \cdot (b_{N-1} \cdots b_0)_{bin}$. According to Eq.(35), the partial product is separated into two parts. The first term is $\frac{1}{2}(b_{N-1}\cdots b_0)_{bin}$. The input $(b_{N-1}\cdots b_0)_{bin}$ is already shifted to $\frac{1}{2}(b_{N-1}\cdots b_0)_{bin}$. Notice that qubits $C_{2N}\cdots C_{-1}$, which store the temporary sum and the final output, is initialized at state $|0\cdots 0\rangle$. Thus, we do not need to apply the full P_{III} to add up $\frac{1}{2}(b_{N-1}\cdots b_0)_{bin}$ and 0. Instead, we can apply a series of CNOT gates, where qubits $B_{N-2} \cdots B_{-1}$ are control qubits, and $C_{N-2} \cdots C_{-1}$ are targets. In the first column of Fig.(10c), the activated qubits in the CNOT series are highlighted. Then consider the other term, $\frac{1}{2}(2a_0-1)(b_{N-1}\cdots b_0)_{bin}$, or equivalently, $-\frac{1}{2}\bar{a}_0 \cdot (b_{N-1}\cdots b_0)_{bin}$. A Pauli-X gate converts qubit A_0 to state $|\bar{a}_0\rangle$. Next, U_{\pm} is applied on qubits $A_0, B_{N-1}, \cdots, B_{-1}$ and D_N, \cdots, D_{-1} , where A_0 corresponds to the sign bit, B_{N-1}, \cdots, B_{-1} correspond to the absolute, and D_N, \dots, D_{-1} are ancilla qubits. By this mean, we get the two's complement representation of signed binary integer $(\bar{a}_0, 0b_{N-1}\cdots b_0)_{bin}$, where \bar{a}_0 is the sign bit. Notice that we have shifted the input, there is an additional 0 (The additional 0 avoids the possible overflow). If $a_0 = 1$, then $\bar{a}_0 = 0$, and U_{\pm} does not change anything. Otherwise, $a_0 = 0$, $\bar{a}_0 = 1$, and U_{\pm} converts qubits B_{N-1}, \cdots, B_{-1} to

Algorithm 6 Algorithm for quantum multiplier based on long multiplication Input: Two N-bit binary integers: $(a_{N-1}\cdots a_0)_{bin}, (b_{N-1}\cdots a_0)_{bin}$ $\begin{array}{l} A_{N-1}, \cdots, A_0 \leftarrow |a_{N-1} \cdots a_0\rangle, \\ B_{N-1}, \cdots, B_0, B_{-1} \leftarrow |b_{N-1} \cdots b_0 0\rangle, \end{array}$ $C_{2N}, \cdots, C_{-1} \leftarrow |0 \cdots 0\rangle,$ $D_{2N-1}, \cdots, D_{-1} \leftarrow |0 \cdots 0\rangle,$ $E_{2N}, \cdots, C_{-1} \leftarrow |0 \cdots 0\rangle.$ (For simplicity, in this Algorithm, qubit A_i is also denoted as B_{N+i}) $n \leftarrow 0.$ while n < N do do SWAP $B_{n-1}, B_n,$ $\mathbf{do}\ n \leftarrow n+1.$ end while $n \leftarrow -1.$ while n < N - 1 do **do** CNOT on B_n (Control), C_n (Target), do $n \leftarrow n+1$. end while do Pauli-X gate on A_0 , **do** U_{\pm} on A_0 (sign bit), B_{N-1}, \cdots, B_{-1} (absolute), D_N, \cdots, D_{-1} (ancilla). do P_{III} on B_{N-1}, \cdots, B_{-1} (input term), C_N, \cdots, C_{-1} (input/output), E_N, \cdots, E_{-1} (ancilla), do CNOT on A_0 (Control), C_N (Target). **do** U^{\dagger}_{\perp} on $A_0(\text{sign bit}), B_{N-1}, \cdots, B_{-1}(\text{absolute}),$ D_N, \cdots, D_{-1} (ancilla). do Pauli-X gate on A_0 . $n \leftarrow 1$. while n < N do $j \leftarrow N$. while j > 0 do do SWAP $B_{n+j-1}, B_{n+j-2},$ do $j \leftarrow j - 1$. end while **do** P_{III} on $B_{N+n-1}, \cdots, B_{n-1}$ (input), C_{N+n}, \cdots, C_{n-1} (input/output), E_{N+n}, \cdots, E_{n-1} (ancilla), do Pauli-X gate on A_n , **do** U_{\pm} on A_n (sign bit), $B_{N+n-1}, \cdots, B_{n-1},$ D_{N+n}, \cdots, D_{n-1} (ancilla). do SWAP $A_n, D_n,$ **do** P_{III} on B_{N+n}, \cdots, B_{n-1} (input), $C_{N+n+1}, \cdots, C_{n-1}$ (input/output), $E_{N+n+1}, \cdots, E_{n-1}$ (ancilla), do SWAP A_n, D_n . do U_{pm}^{\dagger} on A_n (sign bit), $B_{N+n-1}, \cdots, B_{n-1}$, D_{N+n}, \cdots, D_{n-1} (ancilla). **do** CNOT on A_n (Control), $C_N + n$ (Target). do Pauli-X gate on A_n . $n \leftarrow n+1.$ end while $n \leftarrow N$. while n > 0 do do SWAP $B_{n+N-1}, B_{n+N-2},$ do $n \leftarrow n - 1$. end while **Output:** $C_{2N}, \cdots, C_0 \leftarrow |m_{2N} \cdots m_0\rangle$.

the appropriate two's complement representation, corresponding to a negative integer. Then apply P_{III} on qubits $B_{N-1}, \cdots, B_{-1}, C_N, \cdots, C_{-1}$ and E_N, \cdots, E_{-1} , where qubits E_N, \cdots, E_{-1} are ancilla. Notice that the sign bit is not included in this step. At this stage, qubits $C_N, C_{N-1}, \cdots, C_{-1}$ are at state $|00b_{N-1}\cdots b_0\rangle$. P_{III} adds the temporary results up. If $a_0 = 1$, $\bar{a}_0 = 0$, we will have qubits $C_N, C_{N-1}, \cdots, C_{-1}$ at state $|0b_{N-1} \cdots b_0 0\rangle$, corresponding to $(b_{N-1}\cdots b_0)_{bin}$. Otherwise, $a_0 = 0$, $\bar{a}_0 = 1$, we will have qubits $C_N, C_{N-1}, \cdots, C_{-1}$ at state $|10\cdots 0\rangle$, where all digits are 0 except C_N . This result indicates that the temporary sum is 0, and the MSB is 1 as overflow. Till now the sign bit A_0 is excluded in the addition. To take the sign bit into account, we then apply a CNOT gate between qubit A_0 and C_N , where A_0 is control qubit. For $a_0 = 1, \ \bar{a}_0 = 0$, the CNOT gate does not change anything. Whereas for $a_0 = 0$, $\bar{a}_0 = 1$, we will have qubit C_N converted to state $|0\rangle$. Notice that qubits $A_0, B_{N-1}, \cdots, B_{-1}$ are still at the quantum state corresponding to the two's complement representation. We need to reset these qubits. Thus, U_{+}^{\dagger} is applied on qubits $A_0, B_{N-1}, \cdots, B_{-1}$. Then a Pauli-X gate is applied on qubit A_0 , resetting it to the original state $|a_0\rangle$. At end, a series of CNOT gates are applied, shifting up $(b_{N-1} \cdots b_0)_{bin}$ for one digit.

Then consider the partial product $a_1 \cdot (b_{N-1} \cdots b_0)_{bin}.$ In Fig.(10d), the relative activated qubits are highlighted in light blue. We have already shifted the quantum state properly. Qubits $A_1, A_0, B_{N-1}, \dots, B_{-1}$ are at state $|a_10b_{N-1}\cdots b_0a_0\rangle$. Still, the partial product can be separated into two parts, $\frac{1}{2}(b_{N-1}\cdots b_0)_{bin}$, and $-\frac{1}{2}\bar{a}_1 \cdot (b_{N-1}\cdots b_0)_{bin}$. To add up the first part and the temporary sum, P_{III} is applied on qubits $A_0, B_{N-1}, \cdots, B_0, C_{N+1}, \cdots, C_0$, and ancilla qubits E_{N+1}, \cdots, E_0 . Then consider the second term. A Pauli-X gate converts the sign bit A_1 to state $|\bar{a}_1\rangle$, and U_{\pm} is applied to prepare the two's complement representation. Additionally, a SWAP gate is applied, swapping qubits A_1 and D_1 . By this mean, we have qubits A_1 at state $|0\rangle$. At this stage, the temporary sum contains $2^{0} \cdot a_{0} \cdot (b_{N-1} \cdots b_{0})_{bin}$, and $\frac{1}{2} \cdot 2^{1} \cdot a_{1} \cdot (b_{N-1} \cdots b_{0})_{bin}$. Thus, C_{N+1} corresponds to the first non-trivial digit in the temporary $sum(C_{N+2}, \cdots, C_{2N})$ are all at state $|0\rangle$ now). Then P_{III} is applied on qubits $A_1, A_0, B_{N-1}, \cdots, B_0, C_{N+2}, \cdots, C_0$, and ancilla qubits E_{N+2}, \cdots, E_0 . After the addition, the SWAP gate is applied again to swap qubits A_1 and D_1 . Next, a CNOT gate is applied, where A_1 is the control qubit, and C_{N+1} is the target. If $a_1 = 1$, $\bar{a}_1 = 0$, then $\frac{1}{2} \cdot 2^1 \cdot a_1 \cdot (b_{N-1} \cdots b_0)_{bin}$ is added to the temporary sum, and the new temporary sum can be given as $(a_1a_0)_{bin} \cdot (b_{N-1}\cdots b_0)_{bin}$. The product of a two-digit binary number and a

N-digit binary number is no greater than $2^{2+N} - 1$, and can be described by a N + 2 digit binary number. Thus, the temporary sum is stored in qubits C_{N+1}, \dots, C_0 , without any overflow. As $\bar{a}_1 = 0$, the succeeding CNOT gate does not change anything. Otherwise, $a_1 = 0$, $\bar{a}_1 = 1$, then the two's complement representation of $(b_{N-1} \cdots b_0)_{bin}$ is included. Recalling that the summation of $(0b_{N-1} \cdots b_0)_{bin}$ and the two's complement representation of its negative is 2^{N+1} , corresponding to an overflow to the higher order digit. Thus, for $a_1 = 0$, $\bar{a}_1 = 1$, we have the new temporary sum is

$$a_0 \cdot (b_{N-1} \cdots b_0)_{bin} + 2^{N+1}$$

where 2^{N+1} indicates that qubit C_{N+1} is at state $|1\rangle$. As $\bar{a}_1 = 1$, the succeeding CNOT gate reset qubit C_{N+1} to state $|0\rangle$. By this mean, contributions of the product $a_1 \cdot (b_{N-1} \cdots b_0)_{bin}$ cancel out. By the end, we need to reset the relative qubits, and shift the state properly. U_{\pm} and Pauli-X gates are applied again to reset the relative qubits, and a series of CNOT gates are applied for shifting.

The iterative procedures above are repeated for each digit. In Fig.(10e) we present the activated qubits in the calculation of the last partial product $a_{N-1} \cdot (b_{N-1} \cdots b_0)_{bin}$. The first column (from left) in Fig.(10c,d,e) corresponds to the addition of the first term of the partial product. In the second column we highlighted the activated qubits in the preparation of the two's complement representation. Next, the third column corresponds to the addition of the second term of the partial product. In the last column the highlighted qubits are activated for reset and shifting.

After applying the quantum multiplier, we have qubits C_{2N}, \dots, C_0 at state $|m_{2N} \dots m_0\rangle$, where $(m_{2N} \dots m_0)_{bin}$ is the product of the inputs. The ancilla qubits D and E are all reset to state $|0\rangle$. Meanwhile, the quantum multiplier 'swap' the two inputs in the iterative shifting process. By the end, we have qubits B_{N-2}, \dots, B_{-1} at state $|a_{N-1} \dots a_0\rangle$, whereas qubits $A_{N-1}, A_{N-2}, \dots, A_0, B_{N-1}$ at state $|0b_{N-1} \dots b_1 b_0\rangle$. Thus, if the inputs are used in succeeding operations, we still need to reset them by repeating the shifting process.

Then study the time complexity of the proposed quantum multiplier. For each digit, there are four main tasks: shifting, adding up the first term of the partial product, preparing the two's complement representation, adding the second term, and reset. To shift the quantum state up or down for one digit, N CNOT gates are required. Next, the time complexity of quantum adder P_{III} is of the order $\mathcal{O}(N)$. As for the two's complement representation, the time complexity of U_{\pm} is also $\mathcal{O}(N)$. The inputs are both N-digit binary integers, and the tasks above are repeated for N times. Therefore, the overall time complexity of the proposed quantum multiplier is $\mathcal{O}(N^2)$. Similar to P_{III} and U_{\pm} , the proposed quantum multiplier can be implemented using only Pauli-X gates, CNOT gates, and $C\sqrt{X}$ (CSX) gates, and all two-qubit gates are operated between nearest neighbor qubits.

V. QUANTUM DIVIDER

A. Quantum Divider Based on Long Division

Like long multiplication, long division is a standard division algorithm. The first step of long division is to divide the left-most digit of the numerator (dividend) by the denominator (divisor). The quotient (rounded down to an integer) becomes the first digit of the result, and the remainder is then calculated by subtraction. This remainder is then carried forward to the next digit of the dividend, where the division process is reiterated. When all digits have been processed and no remainder is left, the process is complete.

In this section we present a quantum binary divider based on long division algorithm. For given numerator (dividend) $(a_{N-1}\cdots a_0)_{bin}$ and denominator (divisor) $(b_{M-1}\cdots b_0)_{bin}$, our aim is to calculate the quotient $(q_{N-1}\cdots q_0)_{bin}$ and remainder $(r_{M-1}\cdots r_0)_{bin}$. The numerator (dividend) and quotient are N-digit binary integers, whereas the denominator (divisor) and remainder are M-bit binary integers. For simplicity, we can set $M \leq N$ (In fact, even if M > N, we can lengthen the numerator by placing trivial zeros as the first M - N digits). Meanwhile, b_{M-1} can be either 0 or 1. In other words, even if there are trivial zeros in the given denominator, the proposed quantum divider can still work.

Fig.(11a) is a diagram of the required qubits and connectivity for the proposed quantum divider, where each square represents a qubit, and the edges indicate that the nearest neighbor qubits are connected physically. There are in total 5(N +M + 1) qubits. As depicted in Fig.(11a), these qubits are assigned in 5 columns, denoted as D, D'; B, B'; A', A; C', C; E', E, from left to right. In D, D' and B, B' columns, the qubits in the top part are denoted as D or B, and qubits in the bottom part are denoted as D' or B'. On the contrary, in the other three columns, qubit in the top part are denoted as A', C' or E', whereas qubits in the bottom part are denoted as A, C, E. Qubits in the same row share the same subscripts, which indicate their weights in the calculation. Additionally, to implement the full divider, 4 additional qubits D'_{-1} , B'_{-1} , A_{-1} and C_{-1} are required, which are assigned in one row, connected to qubits D'_0 , B'_0 , A_0 and C_0 . If we need the output reminder, then these 4 qubits are necessary. Otherwise, if we only need the output quotient, then we can discard these 4 qubits. Thus for simplicity, we do not plot these 4 qubits in Fig.(11).

In brief, the proposed quantum divider works as follows.

0. Initialization. The input numerator (dividend) $(a_{N-1} \cdots a_0)_{bin}$ is mapped to A', A column, and the denominator (divisor) $(b_{M-1} \cdots b_0)_{bin}$ is mapped to B, B' column. Align the LSB of the divisor, b_0 , and the MSB of the dividend a_{N-1} in the same row.

1. Calculate the two's complement representation of $-(b_{M-1}\cdots b_0)_{bin}$.

2. The division starts from the MSB a_{N-1} . Calculate the summation of a_{N-1} and $-(b_{M-1}\cdots b_0)_{bin}$. Denote the sign bit of the summation is \bar{c}_{N-1} .

3. If the summation is negative, $\bar{c}_{N-1} = 1$, then add up $(b_{M-1} \cdots b_0)_{bin}$ and the temporary sum.

4. If a_{N-1} is not the LSB, then shift the divisor for one digit, aligning b_0 and a_{N-2} in the same row.

5. Repeat 1-4 until all digits have been processed. The quotient is $(c_{N-1} \cdots c_0)_{bin}$, and the dividend has been converted to the remainder $(d_{a_{N-1}} \cdots d_0)_{bin}$ in the iterative subtraction and addition.

Hereafter we present the detailed implementation for each step. At beginning, the given numerator (dividend) $(a_{N-1} \cdots a_0)_{bin}$ is mapped to qubits A_{N-1}, \dots, A_0 , and denominator (divisor) $(b_{M-1}\cdots b_0)_{bin}$ is mapped to qubits B_{M-1},\cdots, B_0 . For the convenience to implement long division, qubits A_{N-1}, \dots, A_0 are assigned in the bottom part of the A', A column, whereas qubits qubits B_{M-1}, \cdots, B_0 are assigned at the top part of the B, B' column. All the other qubits are initialized at state $|0\rangle$. Qubits D, D' and E', E are all ancilla qubits, which will be reset at state $|0\rangle$ after applying the full quantum divider. Qubits C, C' acts like ancilla qubits, yet the output quotient will be stored in these qubits by the end. Notice that b_0 and a_{N-1} are not aligned in the same row yet. To shift the input divisor $(b_{M-1} \cdots b_0)_{bin}$ for one digit, we still need to apply a series of SWAP gates. After the shifting process, we have qubits $B_{M-1}, B_{M-2}, \cdots, B_0, B'_{N-1}$ at state $|0b_{M-1}\cdots b_1b_0\rangle$.

The next step is to calculate the two's complement representation of $-(b_{M-1}\cdots b_0)_{bin}$. Recalling Sec.(III A), operation U_{\pm} can convert the given signed integer to its two's complement representation. Notice that we have shifted the original input $(b_{M-1}\cdots b_0)_{bin}$ for one digit, and qubit B_{M-1} is at state $|0\rangle$ after the shifting process. Thus, we can set qubit B_{M-1} as the sign bit. A Pauli-X gate flips qubit B_{M-1} to state $|1\rangle$, indicating that the signed integer is negative. Next, U_{\pm} is applied on qubits $B_{M-1}, B_{M-2}, \cdots, B_0, B'_{N-1}$ and ancilla qubits $D_{M-1}, D_{M-2}, \cdots, D_0, D'_{N-1}$. By this mean, we have prepared the two's complement representation of $-(b_{M-1}\cdots b_0)_{bin}$. In Fig.(11b) the activated qubits in this step are highlighted with light blue.

Then in step 2, the subtraction $(0 \cdots a_{N-1})_{bin}$ – $(b_{M-1}\cdots b_0)_{bin}$ is calculated. As we have already prepared the two's complement representation of $-(b_{M-1}\cdots b_0)_{bin}$, here we alternatively calculate the summation of $-(b_{M-1}\cdots b_0)_{bin}$ and The summation of these two $(0\cdots a_{N-1})_{bin}$. signed integers can be obtained by applying P_{III} , as discussed in Sec.(IIIB). Operation P_{III} then acts on qubits $B_{M-1}, B_{M-2}, \dots, B_0, B'_{N-1}$ (input), $A'_{M-1}, A'_{M-2}, \dots, A'_0, A_{N-1}$ (input and output), and $E'_{M-1}, C'_{M-1}, C'_{M-2}, \dots, C'_0, C_{N-1}$ (ancilla). The temporary result is store in qubits $A'_{M-1}, A'_{M-2}, \cdots, A'_0, A_{N-1}$ in two's complement representation, where qubit A'_{M-1} is the sign bit. Denote the sign bit of the temporary result as \bar{c}_{N-1} . If $(b_{M-1}\cdots b_0)_{bin} > (0\cdots a_{N-1})_{bin}$, the temporary result is negative, and we have $\bar{c}_{N-1} = 1$. Otherwise $(b_{M-1}\cdots b_0)_{bin} \leq (0\cdots a_{N-1})_{bin}$, and the temporary result is non-negative, we have $\bar{c}_{N-1} = 0$. According to long division, for $(b_{M-1}\cdots b_0)_{bin} >$ $(0 \cdots a_{N-1})_{bin}$, the first digit of the quotient is 0, otherwise 1. Therefore, we have the c_{N-1} as the first digit of the quotient.

In long division, we do the subtraction only if the first digit of the quotient is 1, thus the reminder is always non-negative. However, in the proposed quantum divider, we always calculate the subtraction, and the reminder can be either positive or not. Therefore in step 3, our aim is to add up $\bar{c}_{N-1} \cdot (b_{M-1} \cdots b_0)_{bin}$ and the temporary sum. Recalling Eq.(35), we have

$$\bar{c}_{N-1} \cdot (b_{M-1} \cdots b_0)_{bin} = \frac{1}{2} (b_{M-1} \cdots b_0)_{bin} + \frac{1}{2} (2\bar{c}_{N-1} - 1) (b_{M-1} \cdots b_0)_{bin}$$
(36)

For convenience, in the quantum implementation we add up two alternative terms along with the temporary sum, $\frac{1}{2}(b_{M-1}\cdots b_0)_{bin}$ and $\frac{1}{2}(2\bar{c}_{N-1}-1)(b_{M-1}\cdots b_0)_{bin}$.

Consider the \mathbf{first} term in Eq.(36), By the end of step 2, the $\frac{1}{2}(b_{M-1}\cdots b_0)_{bin}.$ original input $(b_{M-1}\cdots b_0)_{bin}$ has been converted to the two's complement representation of $(-b_{M-1}\cdots b_0)_{bin}$. Thus, U_{+}^{\dagger} is applied to qubits B_{M-1} , B_{M-2} , \cdots , B_0 , B'_{N-1} and ancilla qubits D_{M-1} , D_{M-2} , \cdots , D_0 , D'_{N-1} , resetting qubits B_{M-1} , B_{M-2} , \cdots , B_0 , B'_{N-1} to state $|1b_{M-1}\cdots b_1b_0\rangle$. Then a Pauli-X gate flips qubit B_{M-1} , and the sign bit is flipped from 1 to 0. In Fig.(11d), the activated qubits in the resetting process are highlighted. Next, the divisor is shifted for one digit, corresponding to the amplitude $\frac{1}{2}$ in Eq.(36). Notice that the succeeding summation might change the sign bit of the temporary sum stored in the A', A column, we still need to make a 'copy' of \bar{c}_{N-1} . Thus, four CNOT gates are



FIG. 11: The diagram of connectivity and activated qubits in quantum divider. (a) The required qubits and connectivity for quantum divider. Each square represents a qubit, and the edges indicate that the neighbors are connected physically on a quantum computer. The inputs are mapped to qubits A and B in the second column (from left), whereas the temporary sums and the final output are stored in qubits C in the third column. Qubits D, E in the first and last columns are ancilla qubits. (b-i) The activated qubits involved in the division for the first digit of the dividend (MSB a_{N-1}).

applied, ancilla qubit D_{N-1} is set as state $|\bar{c}_{N-1}\rangle$. The activated qubits in the above process are highlighted in Fig.(11e). Afterward, sum up the shifted divisor and the temporary sum by applying \tilde{P}_{III} , as shown in Fig.(11f). The temporary sum now is the two's complement representation of

$$(0 \cdots a_{N-1} a_{N-2})_{bin} - (b_{M-1} \cdots b_0 0)_{bin} + \frac{1}{2} (b_{M-1} \cdots b_0 0)_{bin} = (0 \cdots a_{N-1} a_{N-2})_{bin} - (b_{M-1} \cdots b_0)_{bin}$$

where the additional 0 indicates that we have shifted the divisor for one digit, and we have $\frac{1}{2}(b_{M-1}\cdots b_0 0)_{bin} = (b_{M-1}\cdots b_0)_{bin}$. Meanwhile, qubit A'_{M-1} stores the information of the sign bit for the temporary sum.

Then consider the contribution of the second term in Eq.(36), $\frac{1}{2}(2\bar{c}_{N-1}-1)(b_{M-1}\cdots b_0)_{bin}$. If $\bar{c}_{N-1} = 1$, $2\bar{c}_{N-1} - 1 = 1$, then our aim is to add up $\frac{1}{2}(b_{M-1}\cdots b_0)_{bin}$. Otherwise, $\bar{c}_{N-1} = 0$, $2\bar{c}_{N-1} - 1 = -1$, then we need to add up $-\frac{1}{2}(b_{M-1}\cdots b_0)_{bin}$. As discussed in Sec.(IV), we can treat the second term as a signed integer, and $2\bar{c}_{N-1} - 1$ corresponds to the sign bit c_{N-1} . After adding up the first term in Eq.(36), we have qubit B_{M-1} at state $|0\rangle$, and ancilla qubit D_{M-1} at state $|\bar{c}_{N-1}\rangle$. Thus, we can swap qubits B_{M-1} and D_{M-1} , then apply Pauli-X gate on qubit B_{M-1} , flipping it

from state $|\bar{c}_{N-1}\rangle$ to $|c_{N-1}\rangle$. Next, U_{\pm} is applied on qubits $B_{M-1}, B_{M-2}, \dots, B_0, B'_{N-1}$ and ancilla qubits $D_{M-1}, D_{M-2}, \dots, D_0, D'_{N-1}$, and the activated qubits are highlighted in Fig.(11g). By this mean, we have qubits $B_{M-1}, B_{M-2}, \dots, B_0, B'_{N-1}$ at the two's complement representation, where qubit B_{M-1} is at state $|c_{N-1}\rangle$, corresponding to the sign bit c_{N-1} . Afterward, \tilde{P}_{III} is applied, adding up the second term and the temporary result, and the activated qubits are highlighted in Fig.(11h).

To add up the two terms in Eq.(36) along with the temporary result, there is one 'unexpected' qubit A_{N-2} involved in the operation \tilde{P}_{III} , as depicted in (11f,h). If $c_{N-1} = 0$, then the total contribution of these two terms is $(b_{M-1} \cdots b_0)_{bin}$, where the LSB b_0 is of the same weight as a_{N-1} . In this case, qubit A_{N-2} is still at state $|a_{N-2}\rangle$ after the summations. Otherwise $c_{N-1} = 1$, then the total contribution of these two terms cancels out. Therefore, the additions do not change the state of qubit A_{N-2} .

Then study the temporary summation. For $\bar{c}_{N-1} = 1$, $c_{N-1} = 0$, we have $(0 \cdots a_{N-1})_{bin} < (b_{M-1} \cdots b_0)_{bin}$. In this case, we add up $(b_{M-1} \cdots b_0)_{bin}$ and the temporary summation, resetting the temporary summation to $(0 \cdots a_{N-1})_{bin}$. $(0 \cdots a_{N-1})_{bin}$ is the reminder for the division of next digit, and the first digit of the quotient is obtained as $c_{N-1} = 0$. On the contrary, if $\bar{c}_{N-1} = 0$, $c_{N-1} = 1$, we have $(0 \cdots a_{N-1})_{bin} \ge 1$

 $(b_{M-1}\cdots b_0)_{bin}$. In this case, the two terms in Eq.(36) cancel out, and the temporary summation is $(0\cdots a_{N-1})_{bin} - (b_{M-1}\cdots b_0)_{bin} \ge 0$. Meanwhile, we have first digit of the quotient is $c_{N-1} = 1$. Till now, we have implemented step 3 and 4. (Notice if a_{M-1} is the last digit of the dividend, and we do not need the output reminder, then step 3 and 4 are not necessary. In this case, the qubits D'_{-1} , B'_{-1} , A_{-1} and C_{-1} are no more necessary.)

By the end, we need to reset the divisor to $(b_{M-1}\cdots b_0)_{bin}$. Thus, U_{\pm}^{\dagger} is applied on qubits $B_{M-1}, B_{M-2}, \cdots, B_0, B'_{N-1}$ and ancilla qubits $D_{M-1}, D_{M-2}, \cdots, D_0, D'_{N-1}$. Besides, SWAP gates are applied on qubits $B_{M-1}, A'_{M-1}, C'_{M-1}$, resetting qubit B_{M-1} to state $|0\rangle$, and converting qubit C'_{M-1} to state $|c_{N-1}\rangle$. Thus, the output quotient is stored in the C', C column.

In Alg.(7) we present the algorithm for quantum divider based on long division. For simplicity, in Alg.(7) qubits B_j , D_j are also denoted as B'_{j+N} , D'_{j+N} , and qubits A'_j , C'_j , E'_j are also denoted as A_{j+N} , C_{j+N} , E_{j+N} . After applying the quantum divider, qubits C_{N+M-1}, \cdots, C_M are converted to quantum state $|q_{N-1}\cdots q_0\rangle$, corresponding to the quotient, a N bit integer denoted as $(q_{N-1}\cdots q_0)_{bin}$. Qubits A_{M-1}, \cdots, A_0 are at state $|r_{M-1}\cdots r_0\rangle$, corresponding to the reminder, a M bit integer $(r_{M-1}\cdots r_0)_{bin}$. Meanwhile, the input divisor is 'shifted', and we have qubits $B'_{M-2}, \cdots, B'_{-1}$ at state $|b_{M-1}\cdots b_0\rangle$. Other qubits in column A', A, B, B' and C', C, along with all ancilla qubits in column D, D' and E', E are at state $|0\rangle$.

At the end of this subsection we would like to give a brief discussion about the time complexity of Alg.(7). In step 1-4, we implement the long division for one single digit of the dividend (specifically, the MSB). We need to repeat these steps for N times, until all digits have been processed. In step 1-4, U_{\pm} (or U_{pm}^{\dagger}) is applied for four times, \tilde{P}_{III} is applied for three times, and we have shifted the divisor for one digit. In total, the time complexity of the proposed quantum divider is of the order $\mathcal{O}(NM)$. As $M \leq$ N, the time complexity is of the order $\mathcal{O}(N^2)$.

B. Division by Zero

In Sec.(VA), both the divisor and the dividend are supposed to be non-negative integers. For inputs without superposition, it is feasible to eliminate the zero divisors. However, the proposed quantum binary divider also supports input with superposition, and we can hardly avoid the zero divisors in the superposition. Thus, we have to face the problematic special case, division by zero, where the divisor (denominator) is zero. Mathematically, the quotient tends to be infinity in this case. Yet in the proposed quantum divisor, the output can never be 'infinity'

Algorithm 7 Algorithm for Quantum Divider Based on Long Division

Input: Two non-negative binary integers: Dividend: $A_{N-1}, \dots, A_0 \leftarrow (a_{N-1} \cdots a_0)_{bin},$ Divisor: $B_{M-1}, \dots, B_0 \leftarrow (b_{M-1} \cdots b_0)_{bin},$ Other qubits are all initialized at state $|0\rangle$ (For simplicity, in this Algorithm, qubits B_j , D_j are also denoted as B'_{j+N} , D'_{j+N} , qubits A'_j , C'_j , E'_j are also denoted as A_{j+N} , C_{j+N} , E_{j+N} .) $j \leftarrow 0$ while j < M do do SWAP on B'_{i+N} , B'_{i+N-1} . do $j \leftarrow j + 1$. end while $n \leftarrow N - 1$ while $n \ge 0$ do do Pauli-X on B'_{M+n} , do U_{\pm} on B'_{M+n} , \cdots , B'_n ; D'_{M+n} , \cdots , D'_n . do \tilde{P}_{III} on B'_{M+n} , \cdots , B'_n ; A_{M+n} , \cdots , A_n ; $C_{M+n}, \cdots, C_n; E_{M+n}, \cdots, D'_n, \cdots, D'_n,$ do U_{\pm}^{\dagger} on $B'_{M+n}, \cdots, B'_n; D'_{M+n}, \cdots, D'_n,$ do Pauli-X on B'_{M+n} . do SWAP on A_{n+N} , B'_{n+N} , do SWAP on B'_{n+N} , D'_{n+N} . $j \leftarrow 0$, while j < M do do SWAP on B'_{n+j} , B'_{n+j-1} . do $j \leftarrow j + 1$. end while **do** P_{III} on $B'_{M+n}, \dots, B'_{n-1}; A_{M+n}, \dots, A_{n-1};$ $C_{M+n},\cdots,C_{n-1};E_{M+n}.$ **do** SWAP on B'_{n+N} , D'_{n+N} , do Pauli-X on B'_{M+n} , \mathcal{D}_{n+N} , \mathcal{D}_{n+N} , do U_{\pm} on B'_{M+n} . do U_{\pm} on B'_{M+n} , \cdots , B'_{n-1} ; D'_{M+n} , \cdots , D'_{n-1} . do \tilde{P}_{III} on B'_{M+n} , \cdots , B'_{n-1} ; A_{M+n} , \cdots , A_{n-1} ; $C_{M+n},\cdots,C_{n-1};E_{M+n}.$ **do** U_{\pm}^{\dagger} on B'_{M+n} , \cdots , B'_{n-1} ; D'_{M+n} , \cdots , D'_{n-1} . **do** SWAP on B'_{M+N} , A_{n+N} , do SWAP on A_{n+N} , C_{n+N} . do $n \leftarrow n - 1$. end while **Output:** Shifted divisor: $B'_{M-2}, \cdots, B'_{-1} \leftarrow |b_{M-1} \cdots b_0\rangle$, Quotient: $C_{N+M-1}, \cdots, C_M \leftarrow |q_{N-1} \cdots q_0\rangle$, Reminder: $A_{M-1}, \cdots, A_0 \leftarrow |r_{M-1} \cdots r_0\rangle$,

rigorously.

Recalling Alg.(7), when the input divisor is 0, the summation of a_{N-1} and $-(b_{M-1}\cdots b_0)_{bin}$ is just a_{N-1} , which is non-negative. Therefore, the first digit of the output quotient is always 1. Then consider the adding back process, according to Eq.(36). As the divisor $(b_{M-1}\cdots b_0)_{bin}$ is 0, both the two terms in Eq.(36) lead to 0 (the two's complement representation for ± 0 is always a string of zeros). Thus, the adding back process does not change the reminder. For positive divisors, each time we do step 1-3, it is guaranteed that the reminder is no greater

than the reminder is less than the divisor, and then we can safely shift the divisor, repeating the calculation for next digit. Yet for zero divisor, the reminder is always no less than the divisor. In this case, MSB of the reminder will be treat as 'sign bit' in the succeeding iteration. Consequently, for zero divisor, the final output quotient of Alg.(7) is $|1\bar{a}_{N-1}\cdots\bar{a}_1\rangle$, and the reminder is $|0\cdots01\rangle$. This result can be problematic. As positive divisors might also lead to the same output quotient and reminder, it is of great difficulty to clarify the normal divisions and the divisions by zero.

To address this issue, here we present a tricky solution. In Alg.(7), the input dividend is a N bit integer $(a_{N-1}\cdots a_0)_{bin}$. We can also treat the input as a N+1 bit integer $(0a_{N-1}\cdots a_0)_{bin}$, where there is an additional 0 as MSB. Thus, the positive divisors always lead to output quotient as a N + 1bit integer, $(0q_{N-1}\cdots q_0)_{bin}$. As the MSB of the input dividend is 0, the MSB of quotient is also 0. On the contrary, for zero divisor, the output quotient is $(10\bar{a}_{N-1}\cdots\bar{a}_1)_{bin}$. To implement this tricky improvement, we only need to delete the first 'while' loop in Alg.(7), and set $n \leftarrow N$ before the second 'while' loop. By this mean, normal divisions lead to output quotient with MSB 0, whereas problematic divisions lead to quotient with MSB 1. Thus, we can distinguish the problematic outputs by testing the MSB.

VI. DISCUSSIONS

For simplicity, in Sec.(1,III,IV,V)we always assume that the inputs are at some certain states in the computational basis. In this section we will demonstrate that the proposed QALUs also support superposition states as input.

Revisit the simplest unit \hat{P}_I , the quantum circuit is as depicted in Fig.(3), and the qubits connectivity is presented in Fig.(2a). The matrix description of \hat{P}_I can be given as

$$\hat{P}_{I} = \begin{pmatrix}
\alpha_{-} & 0 & & & & \\
0 & \alpha_{-} & & & & \\
& & 0 & \beta_{-} & & & \\
& & & \alpha_{+} & 0 & & \\
& & & & \alpha_{+} & 0 & \\
& & & & & \beta_{+} & 0 \\
& & & & & 0 & \beta_{+}
\end{pmatrix}$$
(37)

where α and β are 4×4 matrices,

$$\alpha_{\pm} = \begin{pmatrix} 1 & 0 & 0 & 0\\ 0 & 0 & \frac{1\pm i}{2} & \frac{1\mp i}{2}\\ 0 & 1 & 0 & 0\\ 0 & 0 & \frac{1\mp i}{2} & \frac{1\pm i}{2} \end{pmatrix}$$
(38)

and

$$\beta_{\pm} = \begin{pmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & \frac{1\pm i}{2} & \frac{1\mp i}{2} \\ 1 & 0 & 0 & 0 \\ 0 & 0 & \frac{1\mp i}{2} & \frac{1\pm i}{2} \end{pmatrix}$$
(39)

For simplicity, here the matrix is given in the computational basis. The computational basis are 5 binary digits, corresponding to qubits A, B, C, C', C'', from MSB to LSB, as depicted in Fig.(3). According to Eq.(37), \hat{P}_I does not change the quantum state of A, B (corresponding to the first two digits). Moreover, if the two input terms are different, one at state $|0\rangle$ while the other at state $|1\rangle$, then \hat{P}_I will flip the state of qubit C, which represents the output sum s. The last two digits correspond to the quantum state of qubits C', C''. As discussed in Sec.(II), qubits C', C'' are both initialized at state $|0\rangle$. We have $\alpha_{\pm}|00\rangle = |00\rangle$, and $\beta_{\pm}|00\rangle = |10\rangle$. In other words, α keeps the input $|00\rangle$ as $|00\rangle$, and β flips the input $|00\rangle$ to $|10\rangle$.

Recalling the one-bit quantum full adder with Tofolli gates, as depicted in Fig.(1), the matrix description is

the matrix is also written in the computational basis, corresponding to qubits A, B, C, C', and qubit C' is initialized at state $|0\rangle$. These two operations lead to same output s and c_{out} , when qubits C', C'' are prepared at state $|00\rangle$.

According to Eq.(37), the proposed quantum onebit full adder \hat{P}_{I} supports superposition or entanglement in inputs. Assuming that the input is prepared at a superposition state $\sum_{j,k,l=0,1} \gamma_{j,k,l} |j,k,l,0,0\rangle$, where $\sum_{j,k,l=0,1} |\gamma_{j,k,l}|^{2} = 1$. Then we have the output is also a superposition state,

$$\hat{P}_{I}(A, B, C, C', C'') \sum_{j,k,l=0,1} \gamma_{j,k,l} | j, k, l, 0, 0 \rangle$$

$$= \sum_{j,k,l=0,1} \gamma_{j,k,l} | j, k, s_{j,k,l}, c_{j,k,l}, 0 \rangle$$
(40)

where $s_{j,k,l} = j \oplus k \oplus l$ is the output sum, and $c_{j,k,l} = (j \cdot k) + (l \cdot (j \oplus k))$ is the output carry. The quantum one-bit full adder \hat{P}_I does not change the values of γ . Instead, \hat{P}_I converts the input from one state in the computational basis to another state in the computational basis. Eq.(40) can lead to some

interesting results. For example, if the input is initialized at Bell state[74] (the two input terms are entangled), then we have

$$\hat{P}_{I}\left(\frac{1}{\sqrt{2}}(|0,0,0,0,0\rangle + |1,1,0,0,0\rangle)\right) = \frac{1}{\sqrt{2}}(|0,0,0,0,0\rangle + |1,1,0,1,0\rangle)$$
(41)

where for simplicity, $\hat{P}_I(A, B, C, C', C'')$ is abbreviated as \hat{P}_I . By this mean, the input Bell state is converted to the GHZ state[75, 76], where qubits A, B, C' are entangled.

Then study the another quantum one-bit full adder, \hat{P}_{II} . The quantum circuit of \hat{P}_{II} is depicted in Fig.(4). The matrix description of \hat{P}_{II} is exactly the same as \hat{P}_{I} .

As for P_{III} , the fundamental units are U_C and U_S , as depicted in Fig.(6). U_S is formed by two CNOT gates, whereas the implementation of U_C is more intricate. The matrix description of U_C is

$$U_{C} = \begin{pmatrix} \alpha_{-} & 0 & & & & \\ 0 & \alpha_{-} & & & & & \\ & & \alpha_{+} & 0 & & & \\ & & & 0 & \beta_{-} & & \\ & & & & \alpha_{+} & 0 & \\ & & & & & 0 & \beta_{-} & \\ & & & & & & \beta_{+} & 0 \\ & & & & & & 0 & \beta_{+} \end{pmatrix}$$
(42)

The matrix is expanded in the computational basis. The computational basis are 5 binary digits, corresponding to qubits $A_n, B_n, C_n, C_{n+1}, C_{n+2}$, from MSB to LSB. Qubits C_n, C_{n+1} are prepared at state $|00\rangle$. U_C does never change the state of qubits A_n, B_n, C_n . Thus, the first three digits in the quantum state do not change after applying U_C . The fourth digit, corresponding to the state of qubit C_{n+1} , which re[resents the output carry. The output carry is 1 if there are two or three 1 in the inputs (two input terms, and one input carry), corresponding to the first three digits. Otherwise, the output carry is 0. Therefore, if the first three digits are 011, 101, 110, or 111, U_C flips the fourth digit from state $|0\rangle$ to $|1\rangle$ (corresponding to the β operations in Eq.(42)), otherwise U_C keeps the fourth digit at state $|0\rangle$ (corresponding to the α operations operations in Eq.(42)). The last digit, corresponds to the quantum state of ancilla qubit C_{n+2} . C_{n+2} is initialized at state $|0\rangle$, and the output state of C_{n+2} is also $|0\rangle$. For input superposition state, we have

$$U_{C} \sum_{j,k,l=0,1} \gamma_{j,k,l} | j,k,l,0,0 \rangle$$

$$= \sum_{j,k,l=0,1} \gamma_{j,k,l} | j,k,l,c_{j,k,l},0 \rangle$$
(43)

where $U_C(A_n, B_n, C_n, C_{n+1}, C_{n+2})$ is abbreviated as $U_C, c_{j,k,l} = (j \cdot k) + (l \cdot (j \oplus k))$ is the output carry. The proposed quantum adders P_I, P_{II} and P_{III}

are formed as a cascade of these fundamental units. The quantum adders also support superposition states as input. For P_I , we have

$$P_{I}(A_{N-1}, \cdots A_{0}; C_{N+1}, C_{N}, \cdots, C_{0}; B_{N-1}, \cdots, B_{0}) \sum_{x=0}^{2^{N}-1} \sum_{y=0}^{2^{N}-1} \gamma_{xy} |x_{N-1} \cdots x_{0}; 00 \cdots 0; y_{N-1} \cdots y_{0}\rangle$$

$$= \sum_{i=0}^{2^{N}-1} \sum_{j=0}^{2^{N}-1} \gamma_{ij} |x_{N-1} \cdots x_{0}; 0s_{N} \cdots s_{0}; y_{N-1} \cdots y_{0}\rangle$$
(44)

where $\sum_{i,j=0}^{2^N-1} |\gamma_{ij}|^2 = 1$. For simplicity, the two input integers are denoted as $x, y = 0, 1, \dots, 2^N - 1$, corresponding to the N-bit binary integers $(x_{N-1}\cdots x_0)_{bin}, (y_{N-1}\cdots y_0)_{bin}$, and x_n, y_n are the n^{th} digits. The sum is a N+1 bit binary inte-

ger $(s_N \cdots s_0)_{bin}$. As depicted in Fig.(2c), there are N+2 qubits in the *C* column, whereas the output sum is a N+1 bit binary integer. Thus, there is an additional 0 in the output. For P_{II} , we have

$$P_{II}(A_{N-1}, \cdots A_0; B_{N-1}, \cdots, B_0; C_{N+1}, C_N, \cdots, C_0) \sum_{x=0}^{2^N - 1} \sum_{y=0}^{2^N - 1} \gamma_{xy} |x_{N-1} \cdots x_0; y_{N-1} \cdots y_0; 00 \cdots 0\rangle$$

$$= \sum_{i=0}^{2^N - 1} \sum_{j=0}^{2^N - 1} \gamma_{ij} |x_{N-1} \cdots x_0; y_{N-1} \cdots y_0; 0s_N \cdots s_0\rangle$$
(45)

In P_I , P_{II} , the output sum is stored in a standalone column. P_{III} is a little different, as the output sum-

=

mary is stored in the B column, which represents a input term at beginning. Thus we have

$$P_{III}(A_{N-1}, \cdots A_0; B_N, B_{N-1}, \cdots, B_0; C_N, C_{N-1}, \cdots, C_0) \sum_{x=0}^{2^N - 1} \sum_{y=0}^{2^N - 1} \gamma_{xy} |x_{N-1} \cdots x_0; 0y_{N-1} \cdots y_0; 00 \cdots 0\rangle$$

$$= \sum_{i=0}^{2^N - 1} \sum_{j=0}^{2^N - 1} \gamma_{ij} |x_{N-1} \cdots x_0; s_N s_{N-1} \cdots s_0; 00 \cdots 0\rangle$$

$$(46)$$

Other arithmetic circuits also supports superposition states as input. In Sec.(III), we present the U_{\pm} to calculate the two's complement description of a given signed binary integer, and the quantum circuit of binary subtractor. U_{\pm} contains three main steps: the first step is to flip all bits of the absolute (by applying Pauli-X gate), then add 1 to the inverted result, ignoring the overflow (by applying \tilde{P}_{+1}), and the last step is to reset the ancilla qubits (by applying a series of CNOT gates). The key operation \tilde{P}_{+1} , can be regard as a version of P_{III} , where one input term is set as 1, and the overflow is ignored. For U_{\pm} , we have

$$U_{\pm} \sum_{x=0}^{2^{N+1}-1} \gamma_x | x_N, x_{N-1} \cdots x_0; 0 \cdots 0 \rangle$$

$$= \sum_{x=0}^{2^{N+1}-1} \gamma_x | x_N, \tilde{x}_{N-1} \cdots \tilde{x}_0; 0 \cdots 0 \rangle$$
(47)

where we have $\sum_{x=0}^{2^{N+1}-1} |\gamma_x|^{=1}$, and $U_{\pm}(A_N, \cdots, A_0; C_N, \cdots, C_0)$ is abbreviated as U_{\pm} . The binary description of integer x is a N+1 bit binary integer $(x_N x_{N-1} \cdots x_0)_{bin}$, and we use this binary string to represent a signed integer, where x_N is the sign bit. In this context, $(x_{N-1} \cdots x_0)_{bin}$ is the absolute, and $(\tilde{x}_{N-1} \cdots \tilde{x}_0)$ is the two's complement representation.

With U_{\pm} and the proposed quantum adders, we are able to implement subtraction on quantum computers. Firstly apply U_{\pm} and obtain the two's complement representation of the subtrahend, and then apply P_{III} to sum them up. By this mean, the difference is obtained (in two's complement representation). Nevertheless, U_{\pm} , and the proposed quantum adders, especially P_{III} and \tilde{P}_{III} , constitute the core of the proposed quantum multiplier and divider. The quantum multiplier based on long multiplication, as presented in Alg.(6), is implemented by iteratively applying P_{III} and U_{\pm} , along with shifting from LSB to MSB. Similarly, the quantum divider, as presented in Alg.(7), is implemented by iteratively applying \tilde{P}_{III} and U_{\pm} , along with shifting from MSB to LSB. Like U_{\pm} and P_{III} , the proposed quantum multiplier and divider also support superposition states as input.

VII. CONCLUSION AND OUTLOOK

In this paper, we propose feasible quantum adder, subtractor, multiplier and divider for near-term quantum computers, where the qubits are assigned in two-dimensional arrays. In Sec.(II), we present feasible and scalable quantum full adders P_I , P_{II} for near-term quantum computers, where the input terms are mapped in two columns of qubits, and the output sum is stored in another column of qubits. Moreover, a special quantum adder P_{III} is introduced for iterative additions, where one input column is used to store the output sum. In Sec.(III), we demonstrate the process for obtaining the two's complement representation of a signed binary integer using operation U_{\pm} . The two's complement representation enables subtraction using the proposed quantum adders. Operations P_{III} and U_{\pm} form the core of the proposed quantum multiplier and divider, as discussed in Sec.(IV) and Sec.(V). The processes of long multiplication and division are broken down into iterative shifting, additions, and subtractions. Thus, by iteratively applying P_{III} and U_{\pm} and appropriately shifting temporary results, we can perform multiplications and divisions on quantum computers.

The key features of the proposed QALUs are as follows.

1. Feasibility. The proposed QALUs can be implemented using only Pauli-X gates, CNOT gates and $C\sqrt{X}$ (CSX) gates, and all of the two-qubit gates perform on nearest neighbor qubits. Therefore, the proposed QALUs are feasible for implementation on near-term quantum computers with qubits arranged in two-dimensional arrays.

2. Efficient use of ancilla qubits. In the proposed QALUs, the ancilla qubits are all initialized at state $|0\rangle$, and are reset to state $|0\rangle$ by the end. This allows

for the reuse of ancilla qubits in subsequent operations. Additionally, the circuits avoid the need for extra qubits to store intermediate results, even for complex operations like multiplication and division. **3.** Support for superposition states. As discussed in Sec.(VI), the QALUs are designed to handle superposition states as input. They can process qubits that are in a quantum superposition of multiple states simultaneously. The output of these circuits is also a superposition state, transforming the input from one basis state to another within the computational basis.

We propose specific areas where further investigation could expand upon our work, addressing the limitations identified and exploring new questions that have emerged. The potential directions for future research are as follows.

The minimum requirement of qubit connectivity. The QALUs are designed for quantum computers with a square qubit lattice layout. However, not all advanced quantum computers have this architecture. It is crucial to study the minimum necessary qubit connectivity and determine if the proposed QALUs can function on quantum computers with different architectures, such as IBM's quantum computers.

Readout of superposition outputs and potential quantum speedup. In Sec.(VI), we demonstrate that the proposed QALUs support superposition states as inputs and produce corresponding superposition states as outputs. A critical question is how to efficiently read out and utilize the output superposition states.

Compatibility with quantum error correction techniques. This paper focuses on the feasibility of the QALUs and does not extensively address noise and errors. Advanced quantum error correction techniques are essential for achieving accurate results. Optimizing the proposed QALUs with the assistance of error correction techniques is a meaningful avenue for further research.

From integer to float. In classical computing, floating-point arithmetic (FP) represents subsets of real numbers using an integer with a fixed precision, called the significand, scaled by an integer exponent of a fixed base[77]. Recently, quantum circuits for floating-point addition and multiplication have been proposed, which require long-range two-qubit gates and Toffoli gates [78, 79], making their implementation challenging on near-term quantum computers. This paper focuses on QALUs for integers. An interesting open question is whether the proposed QALUs can be generalized to the FP scheme using Pauli-X gates, CNOT gates, and $C\sqrt{X}$ that operate on neighboring qubits. If the proposed QALUs can be extended to FP arithmetic, they could approximate functions that are difficult to compute, such as exponential functions and logarithms.

In conclusion, we proposes elementary quantum arithmetic logic circuits (QALUs) for performing addition, subtraction, multiplication, and division on near-term quantum computers. These operations are designed to be scalable and feasible for implementation on near term quantum hardware, where qubits are arranged in two-dimensional arrays. The proposed QALUs can be implemented using only Pauli-X gates, CNOT gates and $C\sqrt{X}$ (CSX) gates, and all of the two-qubit gates perform on nearest neighbor qubits. Besides, another key advantage of our approach is the efficient use of ancilla qubits. Ancilla qubits are initialized to the state $|0\rangle$ and are reset to $|0\rangle$ at the end of computations, allowing them to be reused in subsequent operations. This approach reduces the overall number of qubits required, making the circuits more practical for implementation on current quantum hardware, which typically has limited qubit counts. Furthermore, the proposed QALUs support superposition states as input and produce output in superposition states as well. This capability is essential for maintaining the quantum nature of computations and for leveraging the parallelism inherent in quantum computing. The ability to handle superposition states makes these circuits suitable for integration into more complex quantum algorithms. In summary, our work provides feasible, resource-efficient, and scalable methods for performing basic arithmetic operations on near-term quantum computers. The proposed QALUs pave the way toward more complex quantum algorithms and computations.

VIII. ACKNOWLEDGEMENT

J.L gratefully acknowledges funding by National Natural Science Foundation of China (NSFC) under Grant No.12305012.

- D. Deutsch, Quantum theory, the church-turing principle and the universal quantum computer, Proceedings of the Royal Society of London. A. Mathematical and Physical Sciences 400, 97 (1985).
- [2] D. Deutsch and R. Jozsa, Rapid solution of problems by quantum computation, Proceedings of the Royal Society of London. Series A: Mathematical and Physical Sciences 439, 553 (1992).

- [3] E. Bernstein and U. Vazirani, Quantum complexity theory, in *Proceedings of the twenty-fifth annual* ACM symposium on Theory of computing (1993) pp. 11–20.
- [4] S. Lloyd, Universal quantum simulators, Science 273, 1073 (1996).
- [5] A. Ekert and R. Jozsa, Quantum computation and shor's factoring algorithm, Reviews of Modern Physics 68, 733 (1996).
- [6] J. Simon, W. S. Bakr, R. Ma, M. E. Tai, P. M. Preiss, and M. Greiner, Quantum simulation of antiferromagnetic spin chains in an optical lattice, Nature 472, 307 (2011).
- [7] P. Rebentrost, M. Mohseni, and S. Lloyd, Quantum support vector machine for big data classification, Physical review letters 113, 130503 (2014).
- [8] P. M. Preiss, R. Ma, M. E. Tai, A. Lukin, M. Rispoli, P. Zupancic, Y. Lahini, R. Islam, and M. Greiner, Strongly correlated quantum walks in optical lattices, Science **347**, 1229 (2015).
- [9] J. Biamonte, P. Wittek, N. Pancotti, P. Rebentrost, N. Wiebe, and S. Lloyd, Quantum machine learning, Nature 549, 195 (2017).
- [10] J. Preskill, Quantum computing in the nisq era and beyond, Quantum 2, 79 (2018).
- [11] Z. Li, X. Liu, H. Wang, S. Ashhab, J. Cui, H. Chen, X. Peng, and J. Du, Quantum simulation of resonant transitions for solving the eigenproblem of an effective water hamiltonian, Physical Review Letters 122, 090504 (2019).
- [12] Y. Cao, J. Romero, J. P. Olson, M. Degroote, P. D. Johnson, M. Kieferová, I. D. Kivlichan, T. Menke, B. Peropadre, N. P. Sawaya, *et al.*, Quantum chemistry in the age of quantum computing, Chemical reviews **119**, 10856 (2019).
- [13] G. A. Quantum, Collaborators*[†], F. Arute, K. Arya, R. Babbush, D. Bacon, J. C. Bardin, R. Barends, S. Boixo, M. Broughton, B. B. Buckley, *et al.*, Hartree-fock on a superconducting qubit quantum computer, Science **369**, 1084 (2020).
- [14] H.-Y. Huang, M. Broughton, M. Mohseni, R. Babbush, S. Boixo, H. Neven, and J. R. McClean, Power of data in quantum machine learning, Nature communications 12, 2631 (2021).
- [15] E. Altman, K. R. Brown, G. Carleo, L. D. Carr, E. Demler, C. Chin, B. DeMarco, S. E. Economou, M. A. Eriksson, K.-M. C. Fu, *et al.*, Quantum simulators: Architectures and opportunities, PRX quantum **2**, 017003 (2021).
- [16] A. W. Schlimgen, K. Head-Marsden, L. M. Sager, P. Narang, and D. A. Mazziotti, Quantum simulation of open quantum systems using a unitary decomposition of operators, Physical Review Letters 127, 270503 (2021).
- [17] M. Sajjan, J. Li, R. Selvarajan, S. H. Sureshbabu, S. S. Kale, R. Gupta, V. Singh, and S. Kais, Quantum machine learning for chemistry and physics, Chemical Society Reviews 51, 6475 (2022).
- [18] H. Ma, J. Liu, H. Shang, Y. Fan, Z. Li, and J. Yang, Multiscale quantum algorithms for quantum chemistry, Chemical Science 14, 3190 (2023).
- [19] P. W. Shor, Algorithms for quantum computation: discrete logarithms and factoring, in *Proceedings* 35th annual symposium on foundations of computer

science (Ieee, 1994) pp. 124-134.

- [20] A. P. Lund, M. J. Bremner, and T. C. Ralph, Quantum sampling problems, bosonsampling and quantum supremacy, npj Quantum Information 3, 15 (2017).
- [21] A. W. Harrow and A. Montanaro, Quantum computational supremacy, Nature 549, 203 (2017).
- [22] F. Arute, K. Arya, R. Babbush, D. Bacon, J. C. Bardin, R. Barends, R. Biswas, S. Boixo, F. G. Brandao, D. A. Buell, *et al.*, Quantum supremacy using a programmable superconducting processor, Nature **574**, 505 (2019).
- [23] H.-S. Zhong, H. Wang, Y.-H. Deng, M.-C. Chen, L.-C. Peng, Y.-H. Luo, J. Qin, D. Wu, X. Ding, Y. Hu, *et al.*, Quantum computational advantage using photons, Science **370**, 1460 (2020).
- [24] V. Vedral, A. Barenco, and A. Ekert, Quantum networks for elementary arithmetic operations, Physical Review A 54, 147 (1996).
- [25] D. Beckman, A. N. Chari, S. Devabhaktuni, and J. Preskill, Efficient networks for quantum factoring, Physical Review A 54, 1034 (1996).
- [26] A. W. Burks, H. H. Goldstine, and J. Von Neumann, Preliminary discussion of the logical design of an electronic computing instrument, in *The origins of digital computers: Selected papers* (Springer, 1946) pp. 399–413.
- [27] P. Horowitz, W. Hill, and I. Robinson, *The art of electronics*, Vol. 2 (Cambridge university press Cambridge, 1989).
- [28] Y. Takahashi, S. Tani, and N. Kunihiro, Quantum addition circuits and unbounded fan-out, arXiv preprint arXiv:0910.2530 (2009).
- [29] L. Ruiz-Perez and J. C. Garcia-Escartin, Quantum arithmetic with the quantum fourier transform, Quantum Information Processing 16, 1 (2017).
- [30] S. Wang, X. Li, W. J. B. Lee, S. Deb, E. Lim, and A. Chattopadhyay, A comprehensive study of quantum arithmetic circuits, arXiv preprint arXiv:2406.03867 (2024).
- [31] S. A. Cuccaro, T. G. Draper, S. A. Kutin, and D. P. Moulton, A new quantum ripple-carry addition circuit, arXiv preprint quant-ph/0410184 (2004).
- [32] C. Gidney, Halving the cost of quantum addition, Quantum 2, 74 (2018).
- [33] T. G. Draper, S. A. Kutin, E. M. Rains, and K. M. Svore, A logarithmic-depth quantum carrylookahead adder, arXiv preprint quant-ph/0406142 (2004).
- [34] S. Wang and A. Chattopadhyay, Reducing depth of quantum adder using ling structure, in 2023 IFIP/IEEE 31st International Conference on Very Large Scale Integration (VLSI-SoC) (IEEE, 2023) pp. 1–6.
- [35] P. Gossett, Quantum carry-save arithmetic, arXiv preprint quant-ph/9808061 (1998).
- [36] Y. Takahashi and N. Kunihiro, A fast quantum circuit for addition with few qubits, Quantum Information & Computation 8, 636 (2008).
- [37] K.-W. Cheng and C.-C. Tseng, Quantum full adder and subtractor, Electronics Letters 38, 1343 (2002).
- [38] H. Thapliyal and N. Ranganathan, Design of efficient reversible binary subtractors based on a new reversible gate, in 2009 IEEE computer society an-

nual symposium on VLSI (IEEE, 2009) pp. 229–234.

- [39] H. Thapliyal, Mapping of subtractor and addersubtractor circuits on reversible quantum gates, in *Transactions on Computational Science XXVII* (Springer, 2016) pp. 10–34.
- [40] C.-C. Lin, A. Chakrabarti, and N. K. Jha, Qlib: Quantum module library, ACM Journal on Emerging Technologies in Computing Systems (JETC) 11, 1 (2014).
- [41] A. Parent, M. Roetteler, and M. Mosca, Improved reversible and quantum circuits for karatsubabased integer multiplication, arXiv preprint arXiv:1706.03419 (2017).
- [42] E. Muñoz-Coreas and H. Thapliyal, Quantum circuit design of a t-count optimized integer multiplier, IEEE Transactions on Computers 68, 729 (2018).
- [43] S. Kepley and R. Steinwandt, Quantum circuits for f 2[^] n f 2 n-multiplication with subquadratic gate count, Quantum Information Processing 14, 2373 (2015).
- [44] C. Gidney, Asymptotically efficient quantum karatsuba multiplication, arXiv preprint arXiv:1904.07356 (2019).
- [45] S. Dutta, D. Bhattacharjee, and A. Chattopadhyay, Quantum circuits for toom-cook multiplication, Physical Review A 98, 012311 (2018).
- [46] D. S. C. Putranto, R. W. Wardhani, H. T. Larasati, and H. Kim, Space and time-efficient quantum multiplier in post quantum cryptography era, IEEE Access 11, 21848 (2023).
- [47] S. Gayathri, R. Kumar, S. Dhanalakshmi, G. Dooly, and D. B. Duraibabu, T-count optimized quantum circuit designs for single-precision floating-point division, Electronics 10, 703 (2021).
- [48] F. Orts, E. Filatovas, G. Ortega, J. SanJuan-Estrada, and E. Garzón, Improving the number of t gates and their spread in integer multipliers on quantum computing, Physical Review A 107, 042621 (2023).
- [49] H. Thapliyal, E. Munoz-Coreas, T. Varun, and T. S. Humble, Quantum circuit designs of integer division optimizing t-count and t-depth, IEEE transactions on emerging topics in computing 9, 1045 (2019).
- [50] S. Yuan, S. Gao, C. Wen, Y. Wang, H. Qu, and Y. Wang, A novel fault-tolerant quantum divider and its simulation, Quantum Information Processing **21**, 182 (2022).
- [51] F. Orts, R. Paulavičius, and E. Filatovas, Quantum circuit optimization of an integer divider, Journal of Systems and Software **215**, 112091 (2024).
- [52] K. Jang, W. Kim, S. Lim, Y. Kang, Y. Yang, and H. Seo, Quantum binary field multiplication with optimized toffoli depth and extension to quantum inversion, Sensors 23, 3156 (2023).
- [53] Suppressing quantum errors by scaling a surface code logical qubit, Nature **614**, 676 (2023).
- [54] Y. S. Weinstein, M. Pravia, E. Fortunato, S. Lloyd, and D. G. Cory, Implementation of the quantum fourier transform, Physical review letters 86, 1889 (2001).
- [55] D. Coppersmith, An approximate fourier transform useful in quantum factoring, arXiv preprint quantph/0201067 (2002).

- [56] T. G. Draper, Addition on a quantum computer, arXiv preprint quant-ph/0008033 (2000).
- [57] S. Beauregard, Circuit for shor's algorithm using 2n+3 qubits, arXiv preprint quant-ph/0205095 (2002).
- [58] E. Şahin, Quantum arithmetic operations based on quantum fourier transform on signed integers, International Journal of Quantum Information 18, 2050035 (2020).
- [59] C. M. Maynard and E. Pius, A quantum multiplyaccumulator, Quantum information processing 13, 1127 (2014).
- [60] A. Khosropour, H. Aghababa, and B. Forouzandeh, Quantum division circuit based on restoring division algorithm, in 2011 Eighth International Conference on Information Technology: New Generations (IEEE, 2011) pp. 1037–1040.
- [61] Y. Kim, A. Morvan, L. B. Nguyen, R. K. Naik, C. Jünger, L. Chen, J. M. Kreikebaum, D. I. Santiago, and I. Siddiqi, High-fidelity three-qubit i toffoli gate for fixed-frequency superconducting qubits, Nature physics 18, 783 (2022).
- [62] A. Barenco, C. H. Bennett, R. Cleve, D. P. Di-Vincenzo, N. Margolus, P. Shor, T. Sleator, J. A. Smolin, and H. Weinfurter, Elementary gates for quantum computation, Physical review A 52, 3457 (1995).
- [63] N. Yu, R. Duan, and M. Ying, Five two-qubit gates are necessary for implementing the toffoli gate, Physical Review A 88, 010304 (2013).
- [64] E. Smith, M. G. Davis, J. Larson, E. Younis, L. B. Oftelie, W. Lavrijsen, and C. Iancu, Leap: Scaling numerical optimization based synthesis using an incremental approach, ACM Transactions on Quantum Computing 4, 1 (2023).
- [65] J. Li, B. A. Jones, and S. Kais, Toward perturbation theory methods on a quantum computer, Science Advances 9, eadg4576 (2023).
- [66] J. Li, X. Gao, M. Sajjan, J.-H. Su, Z.-K. Li, and S. Kais, M {\o} ller-plesset perturbation theory calculations on quantum devices, arXiv preprint arXiv:2308.01559 (2023).
- [67] M. Y. Siraichi, V. F. d. Santos, C. Collange, and F. M. Q. Pereira, Qubit allocation, in *Proceedings* of the 2018 international symposium on code generation and optimization (2018) pp. 113–125.
- [68] A. Cowtan, S. Dilkes, R. Duncan, A. Krajenbrink, W. Simmons, and S. Sivarajah, On the qubit routing problem, arXiv preprint arXiv:1902.08091 (2019).
- [69] N. M. Linke, D. Maslov, M. Roetteler, S. Debnath, C. Figgatt, K. A. Landsman, K. Wright, and C. Monroe, Experimental comparison of two quantum computing architectures, Proceedings of the National Academy of Sciences **114**, 3305 (2017).
- [70] Q. Zhu, S. Cao, F. Chen, M.-C. Chen, X. Chen, T.-H. Chung, H. Deng, Y. Du, D. Fan, M. Gong, et al., Quantum computational advantage via 60-qubit 24cycle random circuit sampling, Science bulletin 67, 240 (2022).
- [71] C. E. Shannon, A symbolic analysis of relay and switching circuits, Electrical Engineering 57, 713 (1938).

- [72] A. Chaudhuri, M. Sultana, D. Sengupta, and A. Chaudhuri, A novel reversible two's complement gate (tcg) and its quantum mapping, in 2017 Devices for Integrated Circuit (DevIC) (IEEE, 2017) pp. 252–256.
- [73] F. Orts, G. Ortega, and E. M. Garzón, An optimized quantum circuit for converting from signmagnitude to two's complement, Quantum Information Processing 18, 1 (2019).
- [74] M. A. Nielsen and I. L. Chuang, Quantum computation and quantum information (Cambridge university press, 2010).
- [75] D. M. Greenberger, M. A. Horne, and A. Zeilinger, Going beyond bell's theorem, in *Bell's theorem*, quantum theory and conceptions of the universe (Springer, 1989) pp. 69–72.

- [76] N. D. Mermin, Quantum mysteries revisited, Am. J. Phys 58, 731 (1990).
- [77] J.-M. Muller, N. Brisebarre, F. De Dinechin, C.-P. Jeannerod, V. Lefevre, G. Melquiond, N. Revol, D. Stehlé, S. Torres, et al., Handbook of floatingpoint arithmetic, Vol. 1 (Springer, 2018).
- [78] T. Haener, M. Soeken, M. Roetteler, and K. M. Svore, Quantum circuits for floating-point arithmetic, in *International conference on reversible computation* (Springer, 2018) pp. 162–174.
- [79] R. Seidel, N. Tcholtchev, S. Bock, C. K.-U. Becker, and M. Hauswirth, Efficient floating point arithmetic for quantum computers, IEEE Access 10, 72400 (2022).